



Page NO.

1. 1 to 17 – Mid Term
2. 18 to 60- Final Term

MD IFTAKHAR KABIR SAKUR

25th BATCH

COMPUTER AND COMMUNICATION ENGINEERING

International Islamic University Chittagong

COURSE CODE: CCE-2303

COURSE TITLE: Micro Electronics

COURSE TEACHER:

[Abu Zafar Md. Imran](#)

Lecturer

Electronic and Telecommunication Engineering

Feedback Amplifier

08.08.21

7:51 PM

CCE-2303 (Micro Electronics)

E201037
SAKUR

Feedback Amplifier:-

In the process of feedback, a part of output is sampled and fed back to the output input of the amplifier.

In Input we have two signals:

(i) Input signal

(ii) part of the output which is fed back to the input.

Both these signals may be in phase or out of phase.

→ when input signal and part of output signal are in phase, the feedback is called positive feedback.

→ on the other hand, when they are in out of phase, the feedback is called negative feedback.

* Use of positive feedback results in oscillations and hence not used in amplifier.


3.2] Classification OF Amplifiers:-

The classification of amplifiers based on the magnitudes of the input and output impedances of an amplifier relative to the source and load impedances, respectively.

The amplifiers can be classified into four broad categories:-

- (i) voltage
- (ii) current
- (iii) transconductance and
- (iv) transresistance amplifiers.

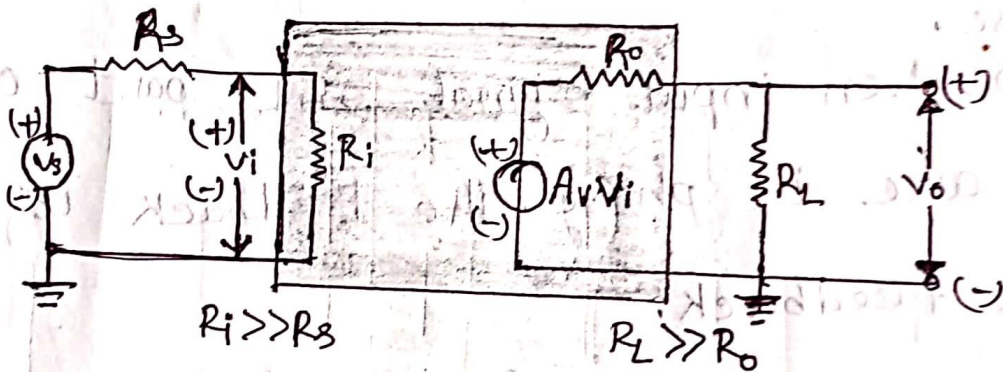(i) Voltage Amplifier:- Figure:- Thevenin's



=> IF the amplifier input resistance R_i is large compared with the source resistance R_s then $v_i = v_s$. IF the external load resistance R_L is large compared with the output resistance R_o of the amplifier, then

$V_o = A_v \cdot V_i = A_v \cdot V_s$ (Such amplifier circuit provides a voltage output proportional to the voltage input and the proportionality factor does not depend on the magnitudes (मूल्य) of the source and load resistances. Hence, this amplifier is called voltage amplifier.) An ideal voltage amplifier must have infinite input resistance (R_i) and zero output resistance (R_o). For practical voltage amplifier we must have $R_i \gg R_s$ and $R_L \gg R_o$

□ Current Amplifier:

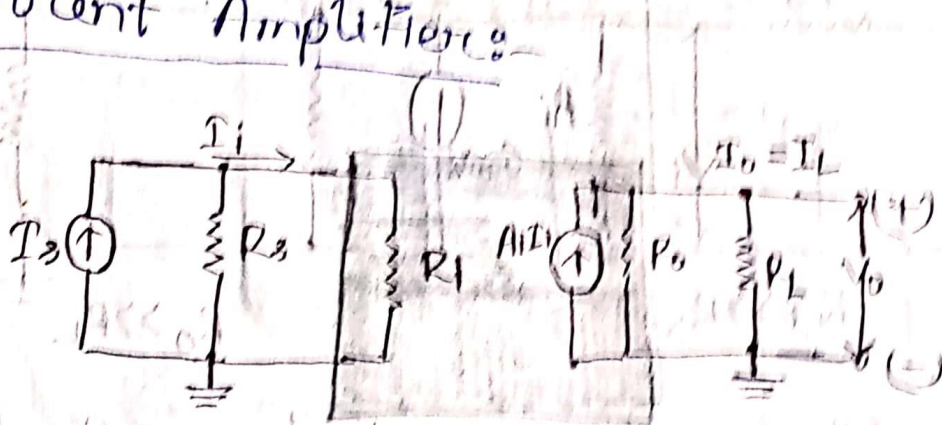


Figure 2. Norton's equivalent circuit of a current amplifier.

\Rightarrow If amplifier input resistance $R_i \rightarrow \infty$, then $I_i = I_s$. If amplifier output resistance $R_o \rightarrow 0$

then $I_L = A_i I_i$. Such amplifier provides a current output proportional to the signal current and the proportionality factor is independent of source and load resistances. This amplifier is called current amplifier.

An ideal current amplifier must have zero input resistance R_i and infinite output resistance R_o . Current amplifier must have $R_i \ll R_s$ and $R_o \gg R_L$.

Transconductance Amplifier

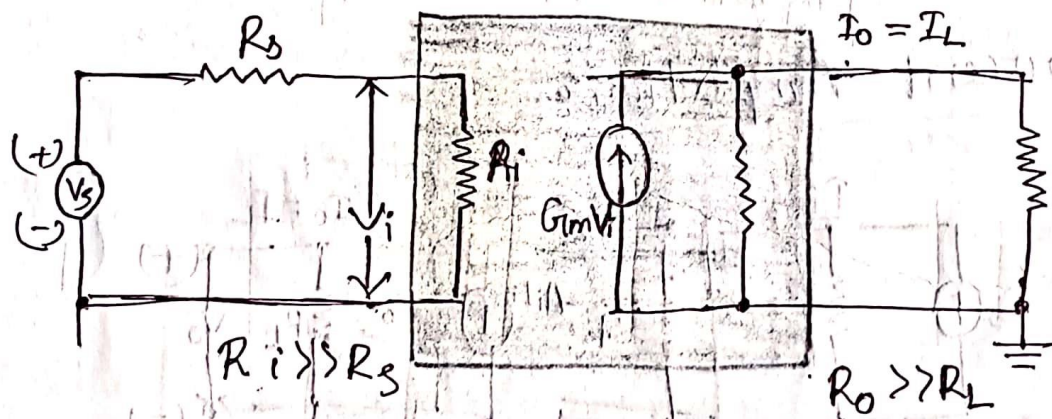


Figure: Transconductance Amplifier

2) Thevenin's equivalent in its input circuit and Norton's equivalent in its output circuit makes transconductance amplifier.

In this amplifier, an output current is proportional to the input signal voltage and the proportionality factor is independent of the magnitudes of the source and load resistances.

Ideally, this amplifier must have an infinite input resistance R_i and infinite output resistance R_o .

For practical transconductance amplifier we must have $R_i \gg R_s$ and $R_o \gg R_L$.

4] Transresistance Amplifier:-

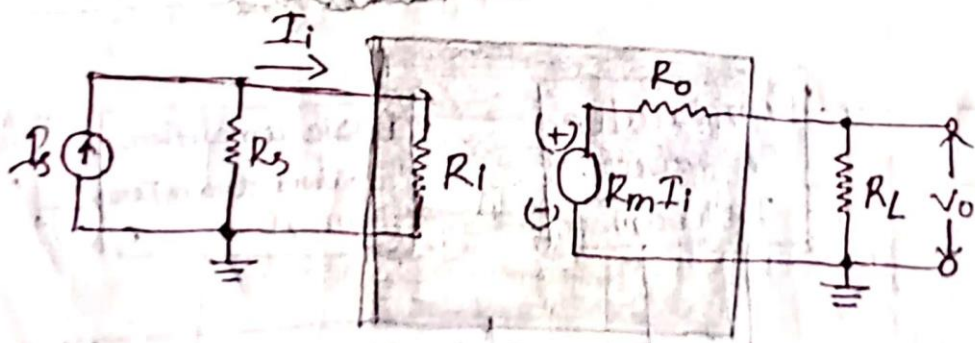


Figure:- Transresistance Amplifier

⇒ A resistance amplifier with a Norton's equivalent in its input circuit. And a Thevenin's equivalent in its output circuit.

In this amplifier an output voltage is proportional to the input signal current and the proportionality factor is independent on the source and load resistances.

Ideally, this amplifier must have zero input resistance R_i and zero output resistance R_o . For practical transistance amplifier we must have $R_i \ll R_s$ and $R_o \ll R_L$.

Feedback Concept

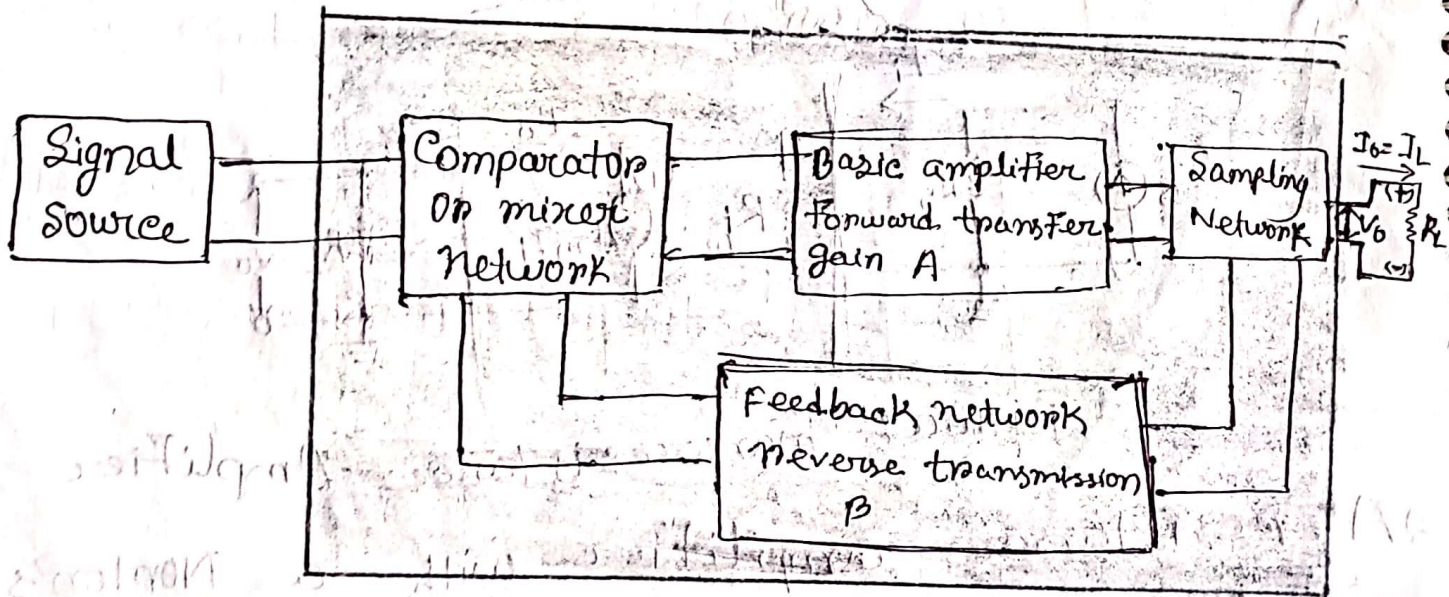


Figure:- Typical Feedback Connection around a basic amplifier


Feedback Connection has three networks:-

- (1) Sampling Network. (নমুনা নেটওয়ার্ক)
- (2) Feedback Network. (প্রতিক্রিয়া নেটওয়ার্ক)
- (3) Mixer Network (মিশ্র নেটওয়ার্ক)

1] Sampling Network:-

There are two ways to sample the output, according to the sampling parameter.

(i) Voltage or Node Sampling:-

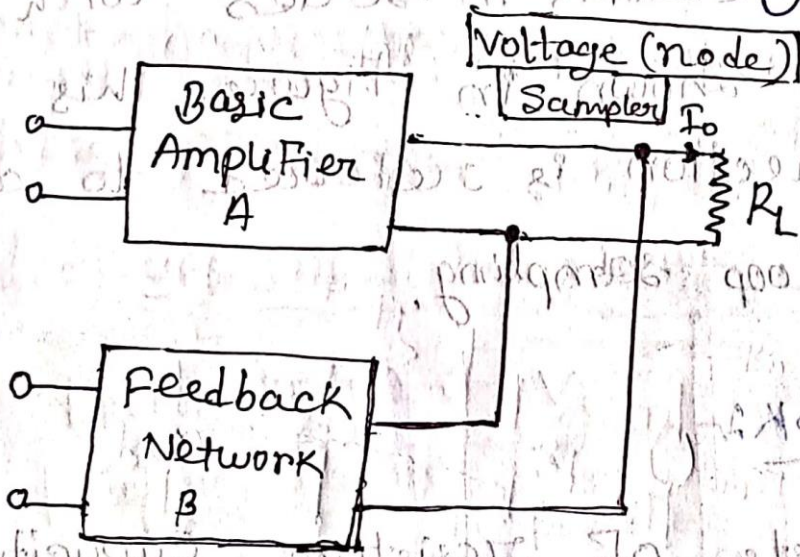

Shunt:-
 A resistor having a very low resistance connected in parallel with other resistor is called shunt.
 The shunt is used in the galvanometer for measuring the large current.

Fig:- Voltage on Node Sampling

=> The output voltage is sampled by connecting the Feedback network in shunt across the output. This connection is referred to as

voltage or node sampling.

(b) Current or loop sampling

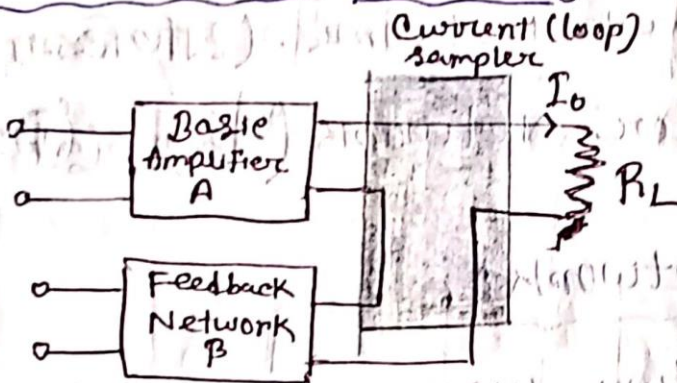


Fig:- Current or loop sampling

\Rightarrow The output current is sampled by connecting the feedback network in series with the output as shown in figure. This type of connection is referred to as current or loop sampling.

[2] Feedback Network:-

It may consist of resistors, capacitors and inductors. Most often it is simply a resistive configuration. It provides reduced provides portion of the output as feedback signal to the the input mixer network.

It is given as,

$$V_f = \beta \cdot V_o$$


Here, β is a feedback factor, or feedback ratio. The which always lies between 0 & 1.

Another β symbol which represent current gain in common emitter amplifier, which is greater than 1. These two β are not same.

3] Mixer Network:-

There are two types of mixer network.

1] Series Input Connection:-

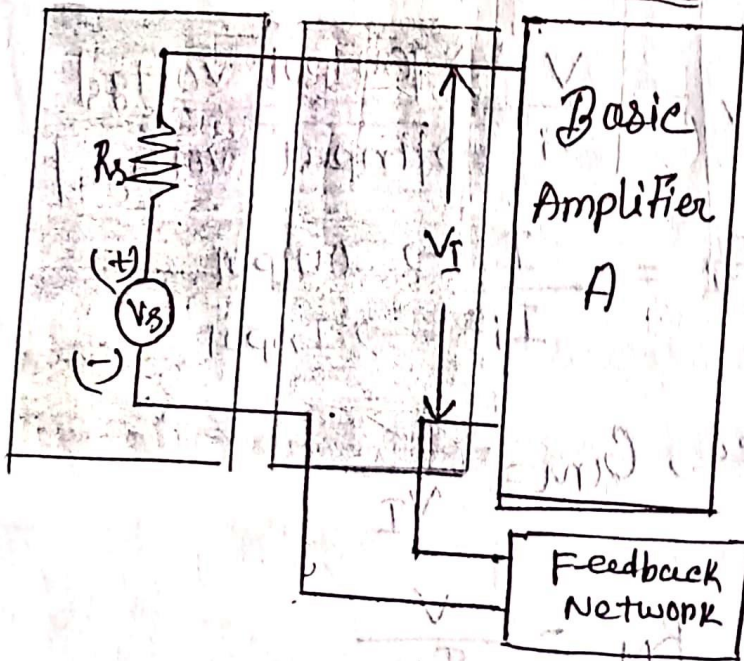

(a) Series mixing

Q2] Shunt Mixing:-

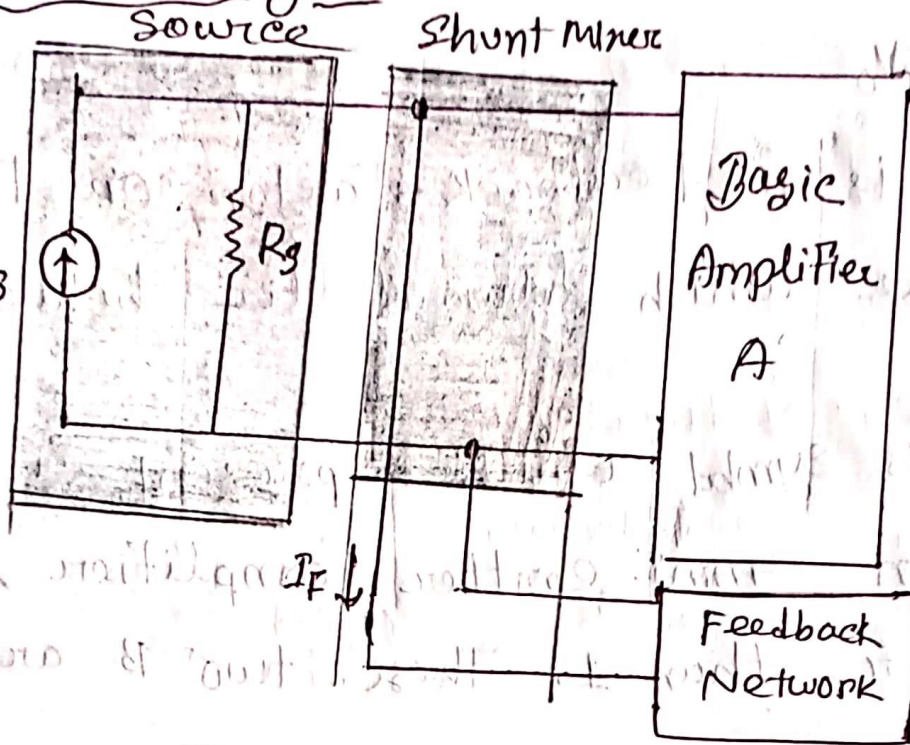


Fig:- Shunt Mixing

Transfer Ratio or Gain:- (without Feedback)

$A =$ The ratio of the output signal to the input signal of the basic amplifier.

① Voltage gain, $A_v = \frac{V_o \rightarrow \text{Output voltage}}{V_i \rightarrow \text{Input voltage}}$

② Current gain, $A_I = \frac{I_o \rightarrow \text{Output}}{I_i \rightarrow \text{Input}}$

③ Transconductance, $G_m = \frac{I_o}{V_i}$

④ Transresistance, $R_m = \frac{V_o}{I_i}$

With Feedback:-

① $A_{VF} =$ (Voltage gain with Feedback)

$$= \frac{V_o \rightarrow \text{Voltage output}}{V_s \rightarrow \text{Signal voltage}}$$

② Current gain with Feedback, $A_{IF} = \frac{I_o \rightarrow \text{output}}{I_s \rightarrow \text{Signal}}$

③ Transconductance with Feedback, $G_{MF} = \frac{I_o}{V_s}$

④ Transresistance with Feedback, $R_{MF} = \frac{V_o}{I_s}$

Negative Feedback Amplifier

When part of output signal and input signal are in out of phase the Feedback is called negative feedback.

The schematic diagram shown figure represents negative feedback because the feedback signal is fed back to the input of the amplifier out of phase with input signal of the amplifier.

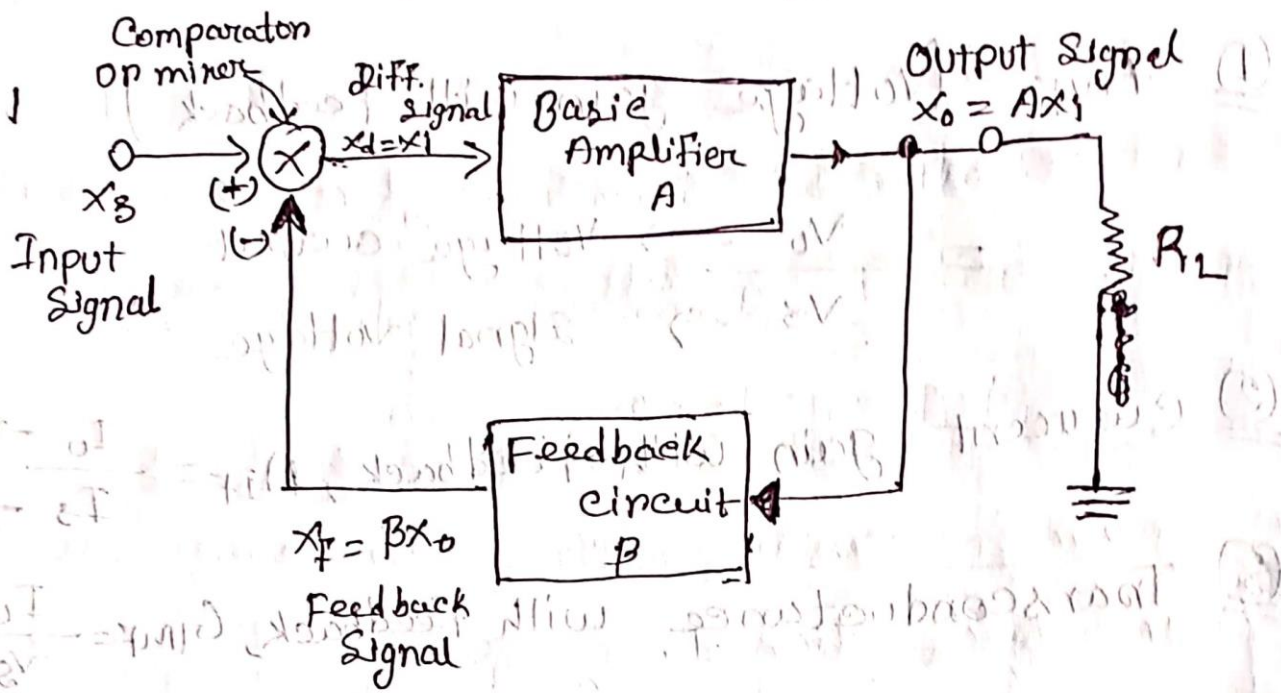


Fig:- Schematic Representation of negative Feedback amplifier.

ways of introducing negative feedback in Amplifiers:-

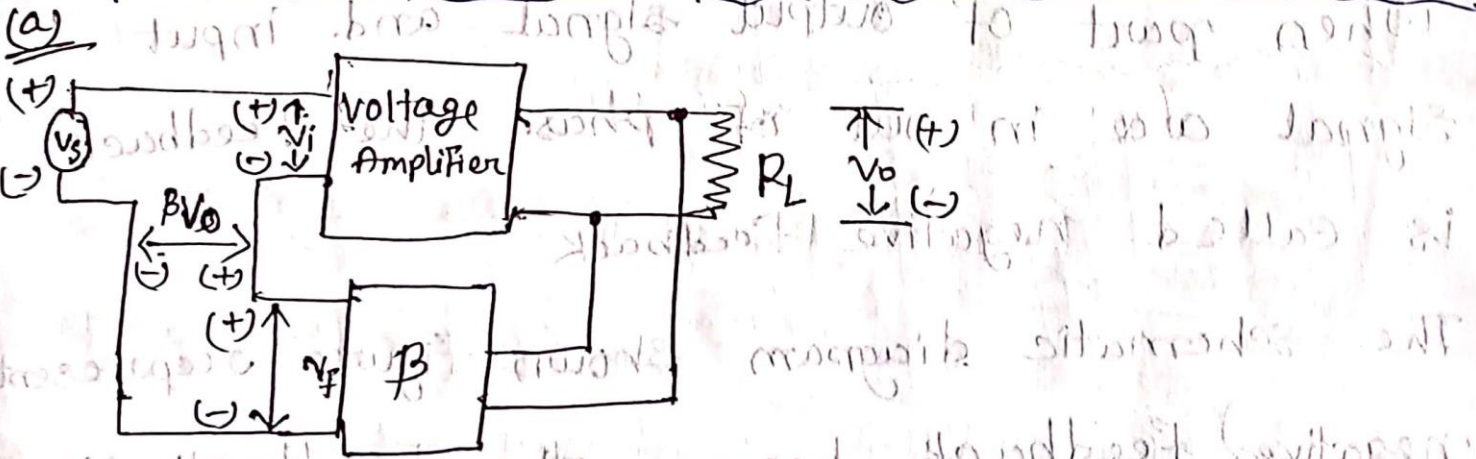


Fig:- Voltage amplifier with voltage series feedback.

16

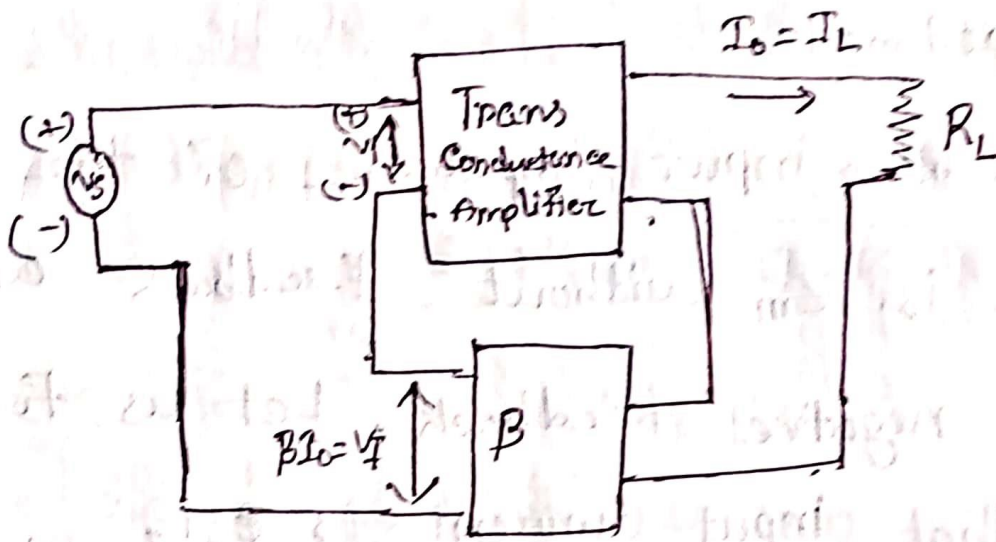


Fig:- Transconductance Amplifier with current series feedback

17

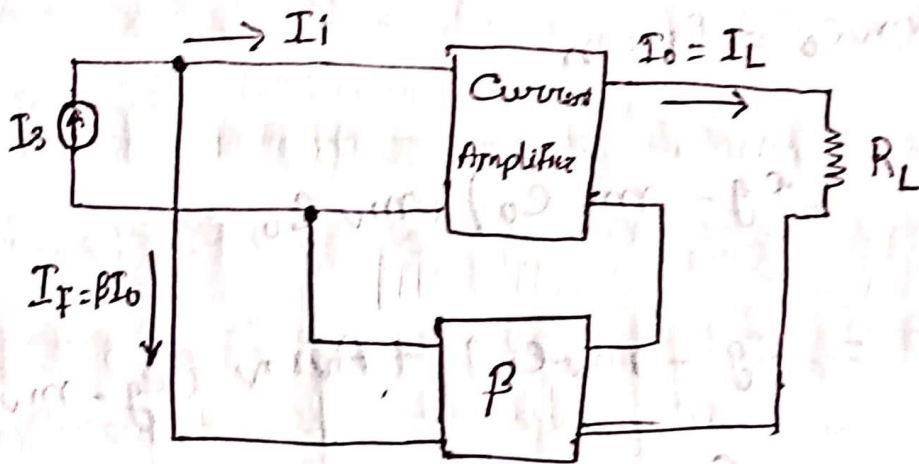


Fig:- Current amplifier with current shunt feedback.

18

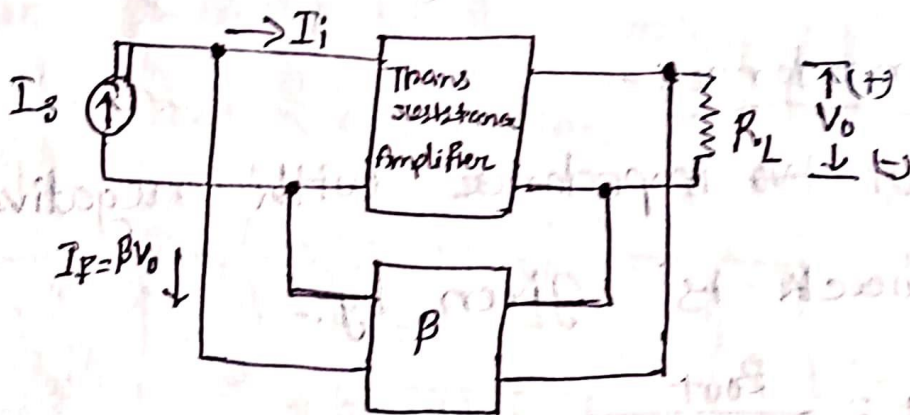


Fig:- Transresistance amplifier with voltage shunt feedback

Input Impedance:-

If the input impedance of the amplifier is Z_{in} without feedback and Z_{in} with negative feedback. Let us further assume that input current is i_1 .

we have,

$$e_g - m v_{e_0} = i_1 Z_{in}$$

$$e_g = (e_g - m v_{e_0}) + m v_{e_0}$$

$$= (e_g - m v_{e_0}) + A_v m v_{e_0}$$

$$= (e_g - m v_{e_0}) (1 + A_v m)$$

$$= i_1 Z_{in} (1 + A_v m)$$

Output Impedance:-

Output impedance with negative voltage feedback is given by:-

$$Z'_{out} = \frac{Z_{out}}{1 + A_v m}$$

Z'_{out} = Output impedance with negative voltage feedback


Z_{out} = Output impedance without Feedback

Oscillators (ऑसिलेटर) (Chapter-4 180 page)


⇒ The positive feedback results into oscillations and hence used in electronic circuit to generate the oscillations of desired frequency. Such circuits are called oscillators.

Concept of positive feedback:-

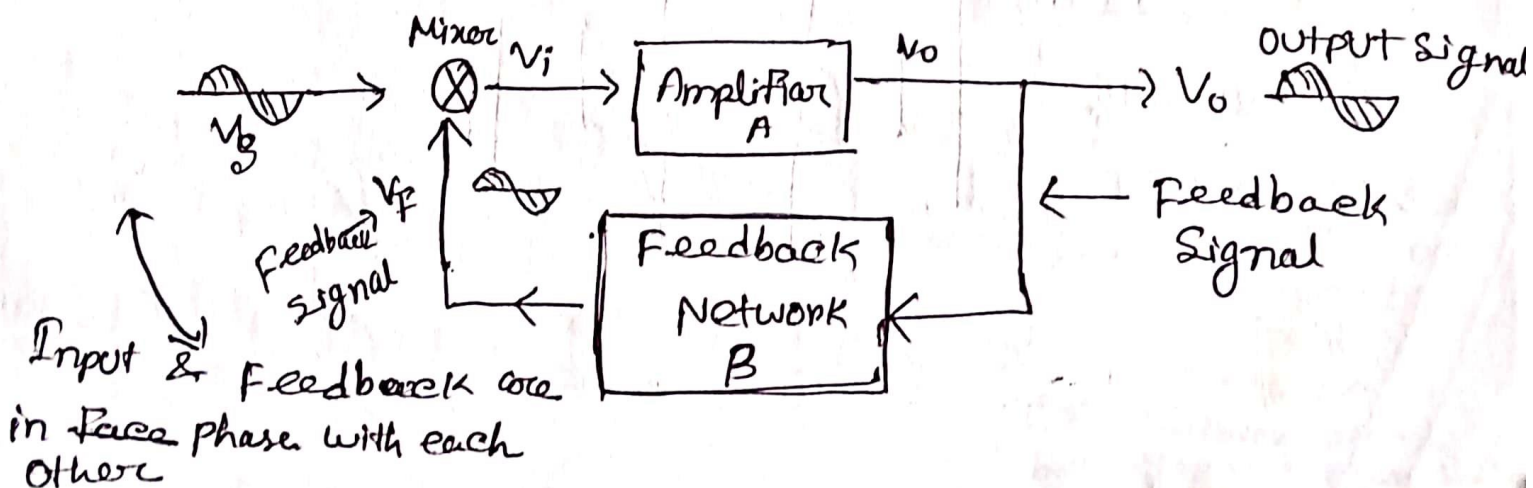The feedback is a property which allows to feedback the part of the output to the same circuit as its input. This is said to be as positive whenever the part of the output that is fed back to the amplifier as its input, is in phase with the original input signal applied to the amplifier.



Assume that a sinusoidal input signal (voltage) V_s is applied to the circuit. An amplifier is non-inverting, the output voltage V_o is in phase with the input signal V_s . The part of the output is fed back to the input with the help of a feedback network. How much part of the output is to be fed back gets decided by the feedback network gain β . No phase change is introduced by the feedback network. Hence the feedback voltage V_f is in phase with the input signal V_s .

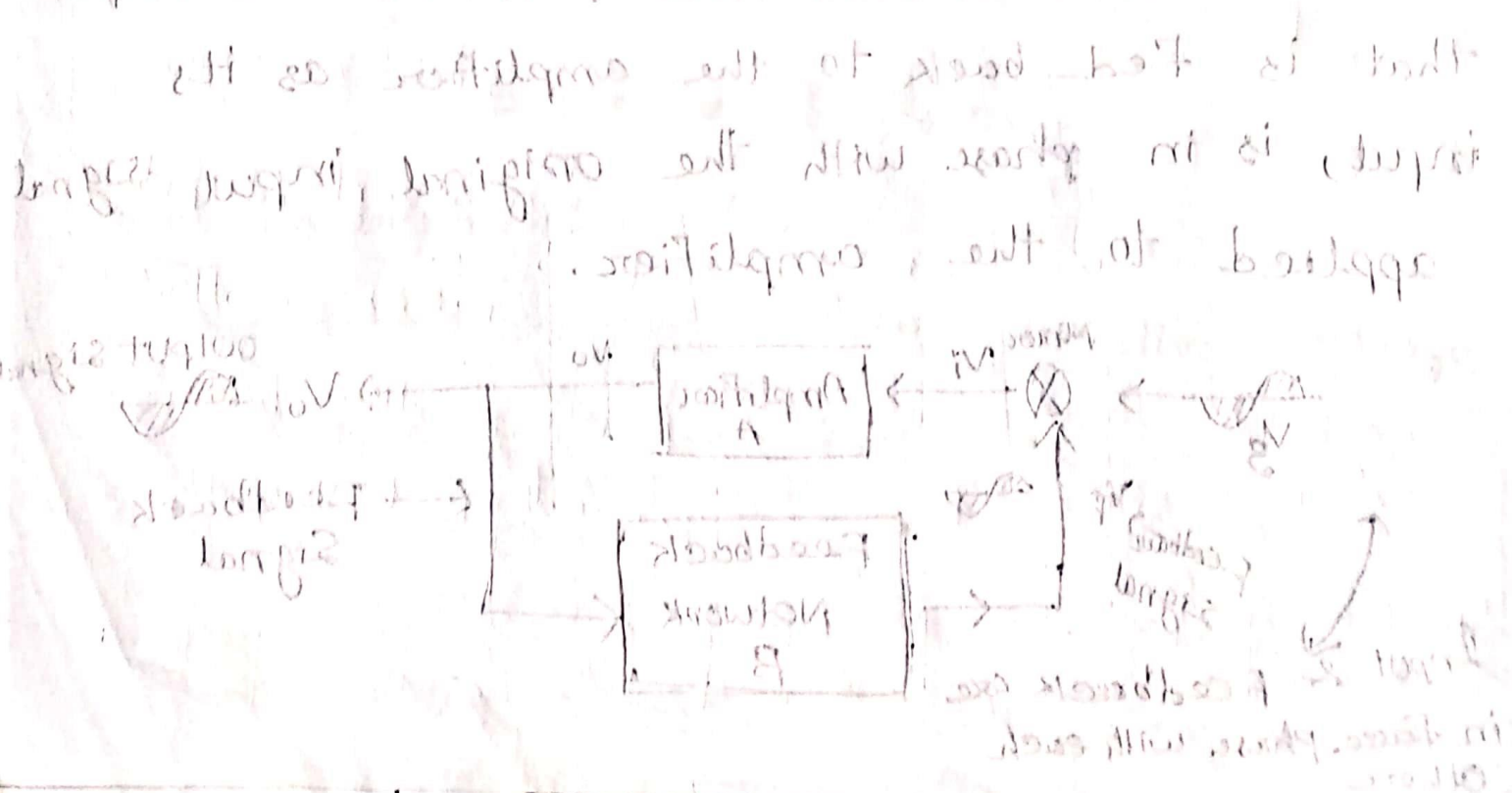

Barkhausen Criterion:-

$$A_{vF} = \frac{A_v}{1 - \beta \cdot A_v}$$

$A_{vF} \equiv$ Voltage gain

With ~~by~~ applying the Feedback Signal (Fb)

Here,

$$\beta \cdot A_v = 0$$

$A_v =$ voltage gain

without Feedback

Fb or, open

Then whole value is 0.

$$A_{vF} = \frac{A_v}{0} \quad \left[\text{The voltage gain with Feedback } (A_{vF}) = \infty \right]$$

loop gain

So, practically not possible

$$A_{vF} = \frac{V_o}{V_{in}}$$

if,

$$A_{vF} = \infty$$

$$V_{in} = 0$$

1st condition OF BC :- Barkhausen criteria


① $\beta \cdot A_v = 1$

[To produce the sustain Oscillation or to produce

un. Oscillation $\rightarrow \beta \cdot A_v = 1$

$180^\circ \rightarrow$ phase shifted

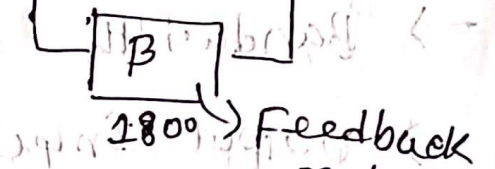② Input \rightarrow A_v \rightarrow Output



\therefore Phases = $180^\circ + 180^\circ = 360^\circ = 0^\circ$

$\leftarrow \beta \cdot A_v = 0^\circ \rightarrow$ The input or Feedback signal

both 0° or 360° Phase shifted



**KEEP
CALM
ITS TIME FOR THE
FINAL
EXAM**

Phase Shift Oscillator


RC Oscillator. → Kind of

Final Exam

Multistage Transistor Amplifiers


PDF: VK Mehra
(P-280)

Cascading :-

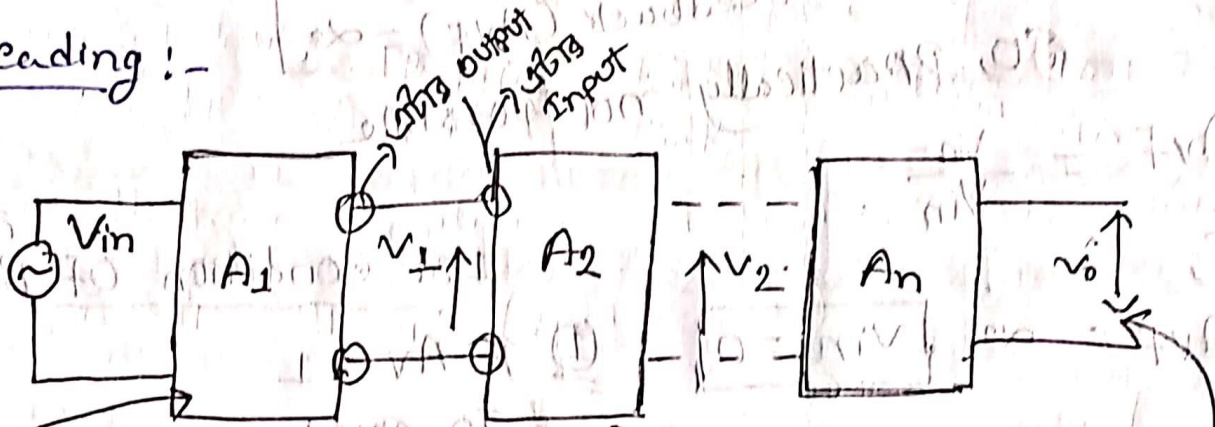

Parameters

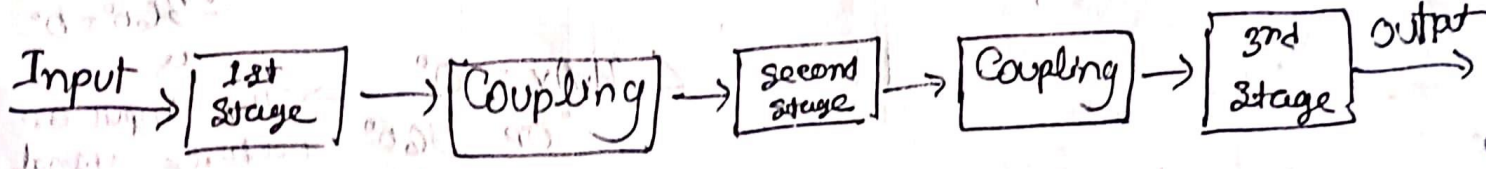- Input Impedance
- Voltage Gain
- Bandwidth
- Output Impedance



Overall Voltage Gain:- (Cascading Configuration)

$$A_v = \frac{V_o \rightarrow \text{voltage output}}{V_i \rightarrow \text{voltage input}}$$

$$A_v = \frac{V_o}{V_{o2}} \rightarrow \text{last Amplifier এর Output}$$

$$\Rightarrow A_v = \frac{V_o}{V_{o2}} \times \frac{V_{o2}}{V_{o1}} \times \frac{V_{o1}}{V_i}$$

\downarrow A_{v3} \rightarrow 3 Amplifier ২টা মনে, \downarrow A_{v2} \rightarrow Amplifier 2 \downarrow A_{v1} \rightarrow amp 1
 Amp 3 \rightarrow voltage gain

$$\Rightarrow A_v = A_{v1} \times A_{v2} \times A_{v3} \quad [\text{মতগুলো Amplifier Connect} \\ \text{তাদের সকলোটার voltage gain এর product}]$$

Overall Current Gain:- এর product]

$$A_i = \frac{I_{o1}}{I_{i1}} \times \frac{I_{o2}}{I_{i2}} \times \frac{I_{o3}}{I_{i3}} \quad [\text{মতগুলো Amplifier} \\ \text{Connect তাদের সকলোটার} \\ \text{Current gain এর product}]$$

\rightarrow Amp 1 \rightarrow Amp 2 \rightarrow Amp 3

$\Rightarrow R_i \rightarrow$ Overall Input Resistance

$\Rightarrow R_o \rightarrow$ Overall output Resistance

Gain in Decibels

① Power Gain, $dB = 10 \log_{10} \left[\frac{P_o / P_i}{\downarrow \downarrow} \right]$ db

Output power Input power

② Overall voltage gain,

$$dB = 20 \log_{10} \left[\frac{v_o / v_i}{\downarrow \downarrow} \right]$$

Output voltage Input voltage
of Amplifier of Amplifier

The common logarithm (log to the base 10) of power gain is known as bel power gain

③ Current gain, $= 10 \log_{10} \frac{I_{out} R}{I_{in} R} = 20 \log_{10} \frac{I_{out}}{I_{in}}$

$\Rightarrow A_v \text{ dB} = A_v \text{ dB}$

* Multistage Amplifier का वोल्टेज गेन

कुल वोल्टेज गेन (Decible में)

$$A_v \text{ dB} = A_{v1} \text{ dB} + A_{v2} \text{ dB} + \dots$$

Gain can happen with current, voltage, power.

$$* G = G_1 \times G_2 \times G_3 \dots \times G_n$$

The gain of multistage amplifier is equal to the product of gains of individual stages.

Transformer Coupling

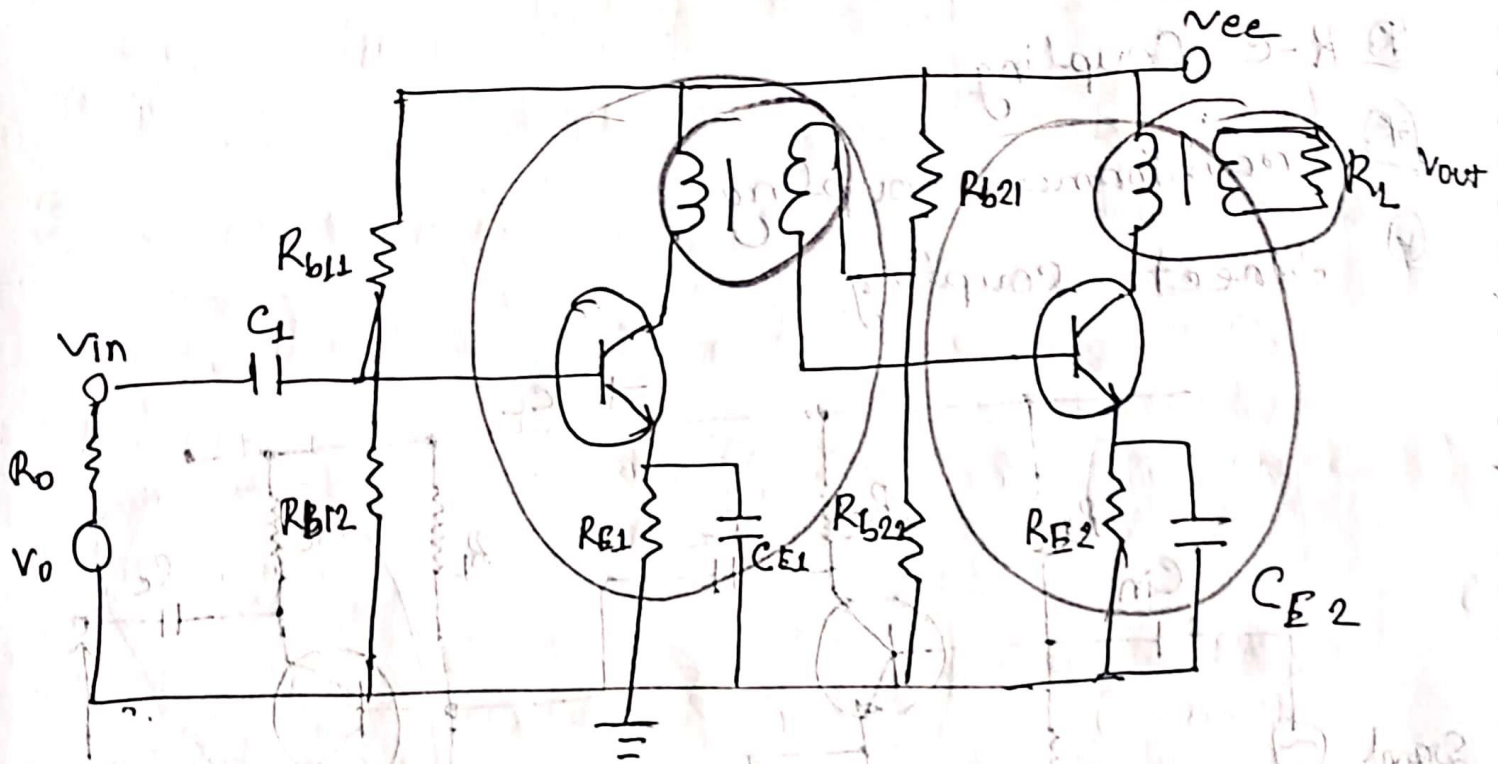


Figure 1 - Transformer coupling

⇒ প্রথমে, দুইটা স্টেজ (0) এর কালেক্ট বস্তায় কন্ড

Transformer use করা হয়েছে। তাই একে

Transformer Coupling বলা হয়।

Direct coupling

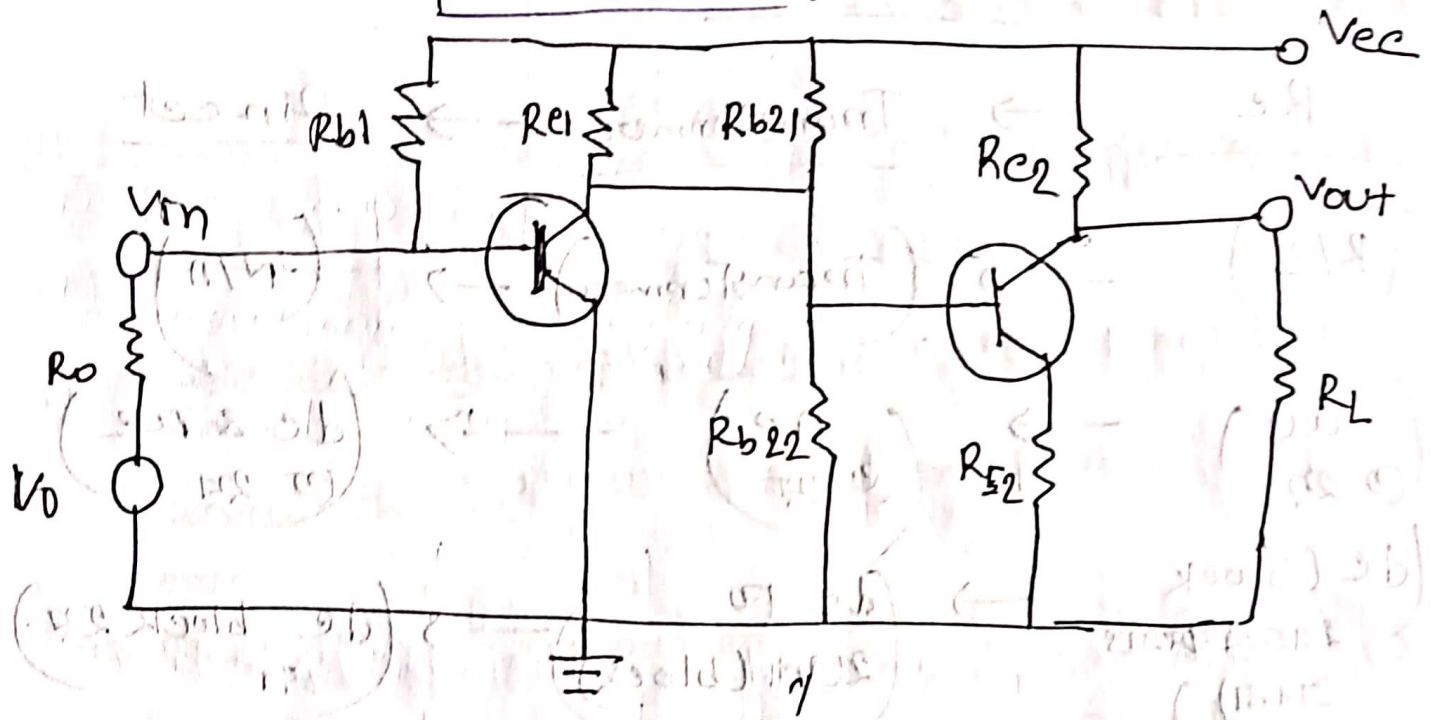


Figure: - Direct coupling

⇒ એવાને R-e વા Transformer લગાવવાને (તેને વગર Direct connect વગર શરૂ કરે) તેને Direct coupling

Difference

Re

Transformer

Direct

- | | | |
|---|-----------------------------------|------------------------------------|
| <p>① (Re)</p> | <p>→ (Transformer)</p> | <p>→ (N/A)</p> |
| <p>② (ac
ଅନୁ)
(ଅନୁ)</p> | <p>→ (ac
ଅନୁ)</p> | <p>→ (dc & ac
ଅନୁ ଅନୁ)</p> |
| <p>③ (dc block
ଅନୁ ଅନୁ
ଅନୁ)</p> | <p>→ (dc ଅନୁ
ଅନୁ (block))</p> | <p>→ (dc block ଅନୁ
ଅନୁ)</p> |
| <p>④ De ଅନୁ
Amplification ଅନୁ</p> | <p>← (Same)</p> | <p>← (Same)</p> |

Frequency Response & Bandwidth

⊛ Lower 3dB Frequency of a cascaded multistage Amplifier:-

⇒ Cascade of n cascaded multistage

bandwidth 2ω or less than 2ω

starts,

→ Multistage Amplifier or Bandwidth,

Singlestage Amplifier 2ω or 2ω

⇒ Single stage > Multistage

$$\therefore \text{Bandwidth} = f_H(L) - f_L(n) \rightarrow \text{①}$$

Here,

$f_L(n)$ → Lower 3dB Frequency


$$\Rightarrow f_L(n) = \frac{f_L}{\sqrt{2^{1/n} - 1}} \rightarrow \text{Lower Single stage amplifier lower 3dB Frequency}$$

$n = \text{number of stages connected}$

⊛ The voltage gain of an amplifier varies with single frequency. Because the reactance of the capacitors in the circuit changes with signal frequency. The curve between voltage gain & signal frequency of an amplifier is known as frequency response.

Upper 3dB Frequency :-


$$F_H(n) = F_H \sqrt{2^{1/n} - 1}$$

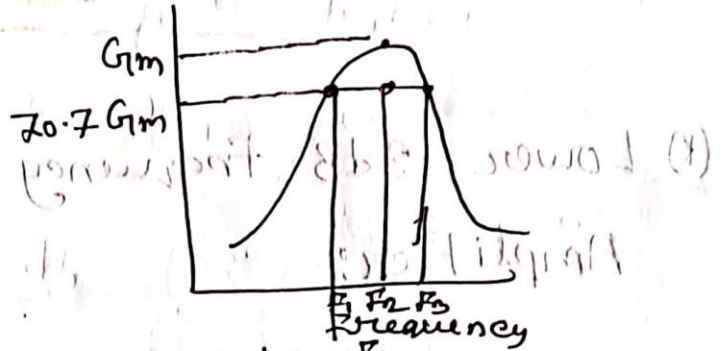

F_H = Single Stage Upper 3dB Frequency

n = no. of stage

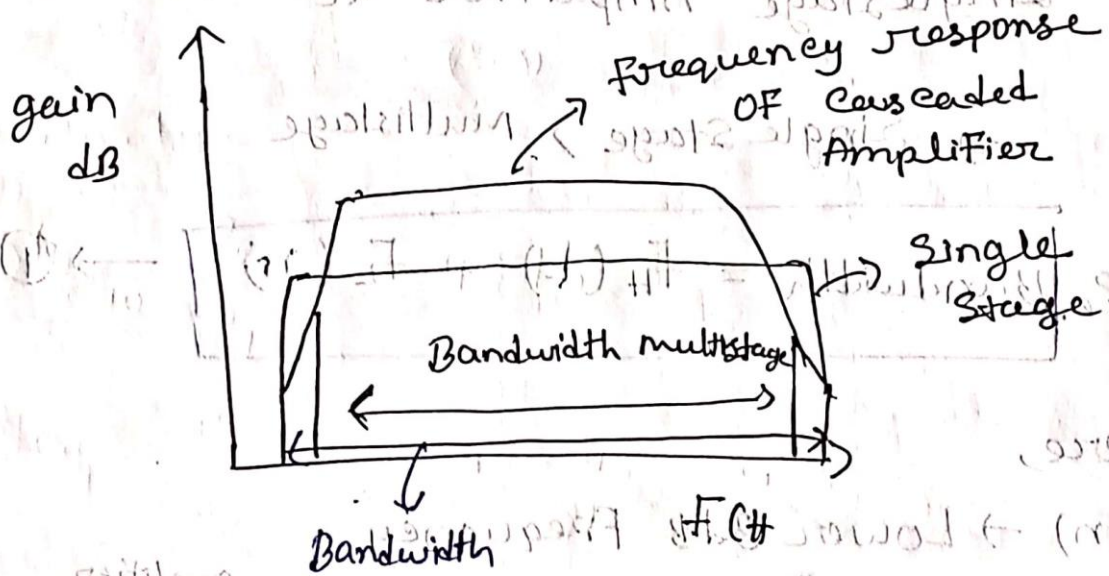Bandwidth of Cascaded multistage Amplifier :-



So, $\text{Bandwidth} = F_H(n) - F_L(n)$

Bandwidth :- The range of frequency over which the voltage gain is equal to or greater than 70.7% of the maximum gain is known as Bandwidth.

Bypass Capacitors

A bypass capacitor is connected in parallel with a circuit to bypass the a.c signal and hence the name.

Find the gain in dB

Math on (pdf: vk-mehta page: 285)

① voltage gain 30

$$= 20 \log_{10} 30 \text{ dB}$$

$$= 29.54 \text{ dB}$$

② power gain 100

$$= 10 \log_{10} 100$$

$$= 20 \text{ dB}$$

Express the gain in number:-

① power gain of 40 dB

$$= \text{power gain} = 40 \text{ dB} = 4 \text{ bel}$$

[IF we want to find the gain as a number, we should work from logarithm back to the original number.]

∴ Gain = Antilog 4 = 10⁴ = 10,000

(ii) power gain of 43 db

= power gain = 4.3 bel

= Antilog 4.3 = 2 × 10⁴ = 20,000

(Ans)

Alternatively:-

$$10 \log_{10} \frac{P_2}{P_1} = 43 \text{ db}$$

$$\Rightarrow \log_{10} \frac{P_2}{P_1} = \frac{43}{10} = 4.3$$

$$\Rightarrow \frac{P_2}{P_1} = (10)^{4.3} = 20,000$$

Format:-

$$\frac{V_2}{V_1} = (10)^{\frac{\text{gain in db}}{20}}$$

$$\frac{P_2}{P_1} = (10)^{\frac{\text{gain in db}}{10}}$$

⊛ An amplifier has an open-circuit voltage gain of 70 db & an output resistance of

1.5 k Ω . Determine the minimum value of

load resistance so that voltage gain is not

more than 67 db.

Open circuit
 \Rightarrow voltage gain, $A_o = 70 \text{ db}$

Output Resistance, $R_o = 1.5 \text{ k}\Omega$

voltage gain, $A_v = 67 \text{ db}$

So,

$$20 \log_{10} A_o - 20 \log_{10} A_v = 70 - 67$$

$$\text{Or, } 20 \log_{10} \frac{A_o}{A_v} = 3$$

$$\text{Or, } \log_{10} \frac{A_o}{A_v} = \frac{3}{20}$$

$$\text{Or, } \frac{A_o}{A_v} = (10)^{\frac{3}{20}}$$

$$\text{Or, } \frac{A_o}{A_v} = 1.413$$

$$\text{But, } \frac{A_v}{A_o} = \frac{R_o}{R_o + R_L}$$

$$\text{or, } \frac{1}{1.41} = \frac{R_L}{1.5 + R_L}$$

$$\therefore R_L = 3.65 \Omega$$

(Ans)

Properties of db gain:

(i) Each time the ordinary power gain increases/decreases by a factor of 10, the db power gain increases/decreases by 10 db.

$$\therefore \text{Increase in db power gain} = 10 \log_{10} 1000 - 10 \log_{10} 100$$

$$= 30 - 20 = 10 \text{ db}$$

(ii) Each time the ordinary power gain increases/decreases by a factor of 2, the db power gain increases/decreases by 3db.

For example, suppose the (power) gain increases from 100 to 200

$$\therefore \text{Increase in db power gain} = 10 \log_{10} 200 - 10 \log_{10} 100$$

$$= 23 - 20$$

$$= 3 \text{ db}$$


Q when there is an even number of cascaded stages (2, 4, 6, ...) the output signal is not inverted from the input.

→ when there is an odd number (1, 3, 5, ...) the output signal is inverted from the input.

[आउट Math पर]

Transistor AUDIO Amplifier } Pdf: vk-mehla Page -> 306

Large Signal Amplifier

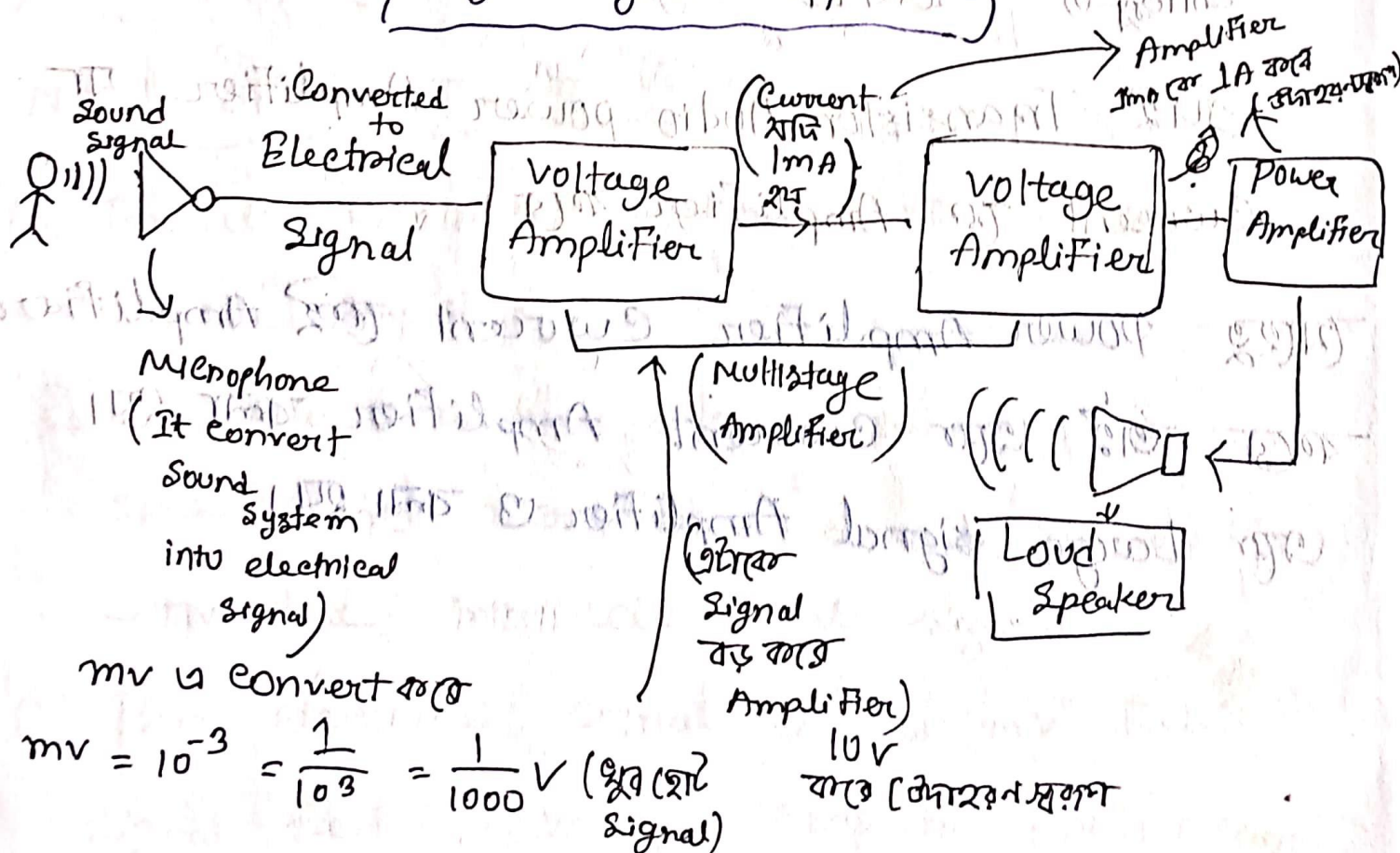

$$So, P = VI$$

$$\Rightarrow 10W (watt) = 10V \times 1A$$

$$P = 10VA$$

$$P = 10W (watt)$$

অতঃপর এই 10W (watt) এর signal Loud speaker এ মাঝে একে এ পরিমাণ sound বের হবে।

যদি, power Amplifier নাগানো না হতো যত volt এর signal -ই দেওয়া হোক না কেনো কার্যকর sound signal পাওয়া যেতো না।

এটাই Transistor Audio power Amplifier যা Current এর Amplifier বলে।

যেহেতু power Amplifier current এর Amplifier বলে তাই একে Current Amplifier বলা হয়।

এক Large signal Amplifier ও বলা হয়।

Audio \rightarrow 20 Hz to \sim 20 KHz or 20,000 Hz

এই Range এর ডিওর আমরা ক্ষুণ্ণ পাতি। আর এই
সিগনাল কেই Amplify করে আর একেই বলা
হয় power Amplifier.

Transistor Audio power Amplifier:-

Is a special Amplifier is a device or
amplifier which amplify (raise) power level
of the signal with audio range we call
as TAPA (Transistor Audio--).

Need of power Amplifier:-


- ① In all Electrical system, last stage is power Amplifier.
- ② In public address system, when a person speaks into microphone, sound signal is converted into electrical signal.
- ③ This electrical signal is few mv. This signal fed to voltage Amplifier (Multistage Amplifier) which amplifies weak signal

and amplify in mV level to volt (signal)

④ But loudspeaker requires sufficient power

level, so we use power amplifier which amplify power level (Amplify current)

$$P = V I$$

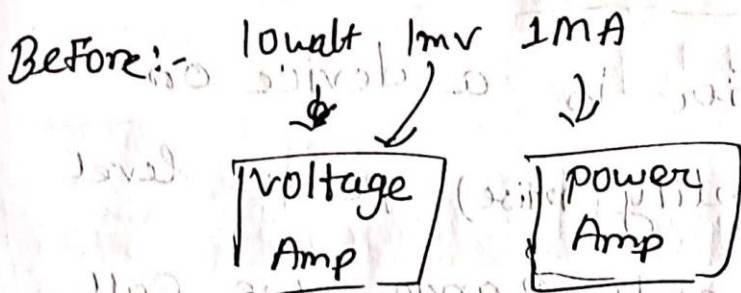


After:-

$$10 \text{ V} \times 1 \text{ A} = 10 \text{ VA}$$

$$\therefore P = 10 \text{ watt}$$

Regulated DC power Supply

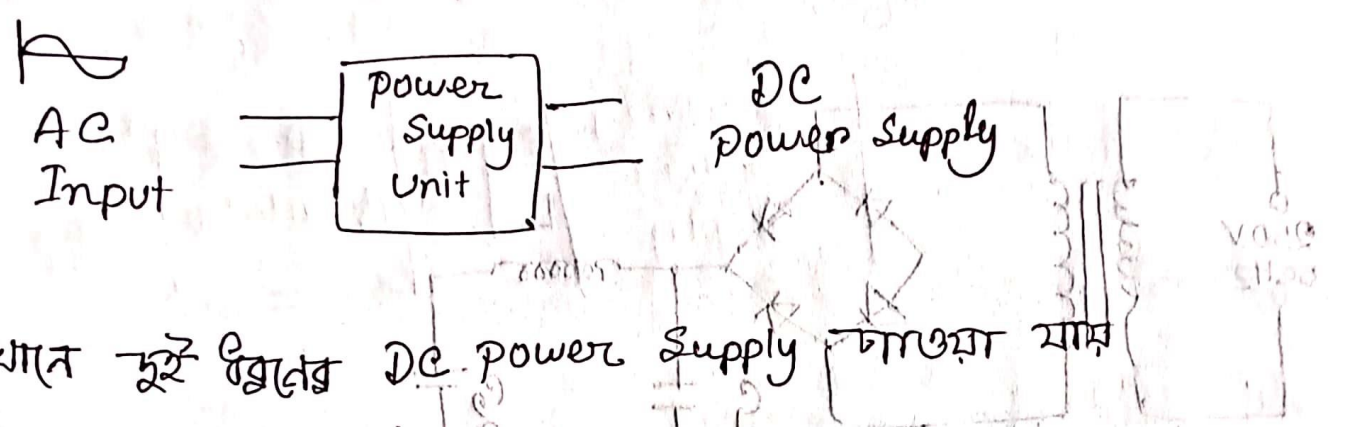DC power supply হল AC থেকে DC - তে রূপান্তর করা হয়।




এখানে দুই প্রকার DC power supply পাওয়া যায়

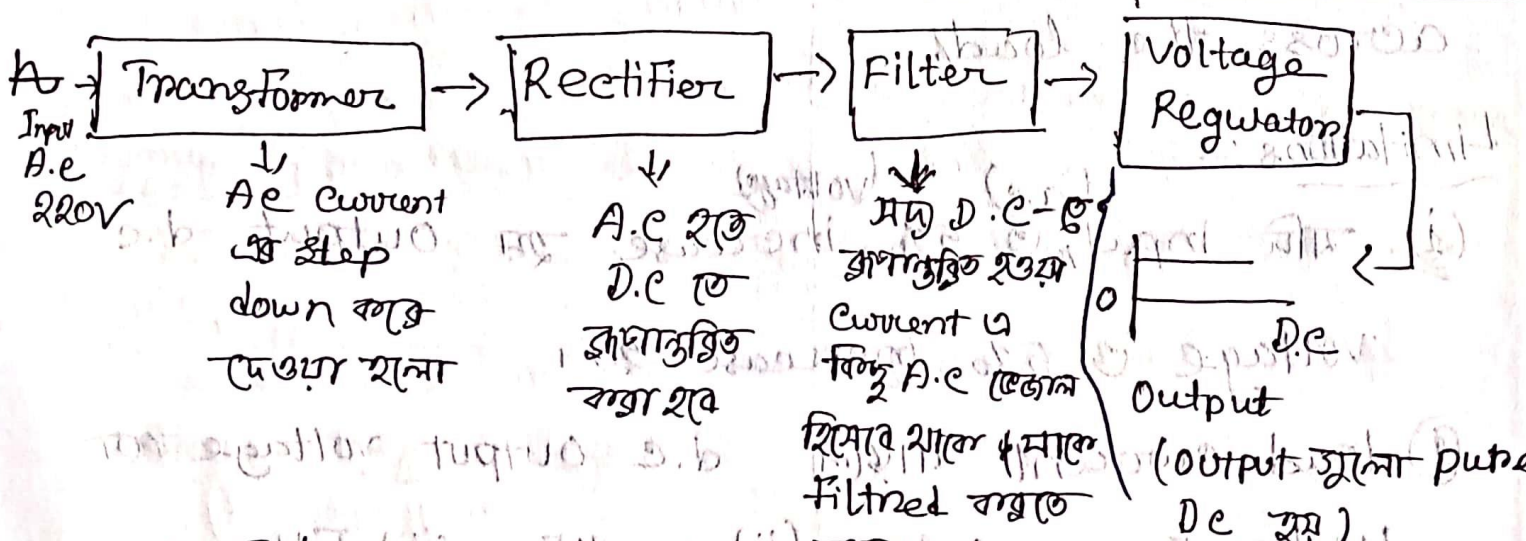- (i) Regulated P.S. (Filtering করা এমন)
- (ii) Unregulated P.S. (" " নাম " ")

Block Diagram

Transformer - এ Current উঠে- নামা করলে Output এর DC তেও অসামঞ্জস্যতা থাকবে যা circuit এর জন্য ক্ষতি। তাই voltage Regul. d. circuit ব্যবহার করা হয়।



Use:- Television, Computer

Ordinary DC Power Supply

(An ordinary DC power supply)

An ordinary, unregulated DC power supply contains a transformer, a rectifier, a filter circuit.

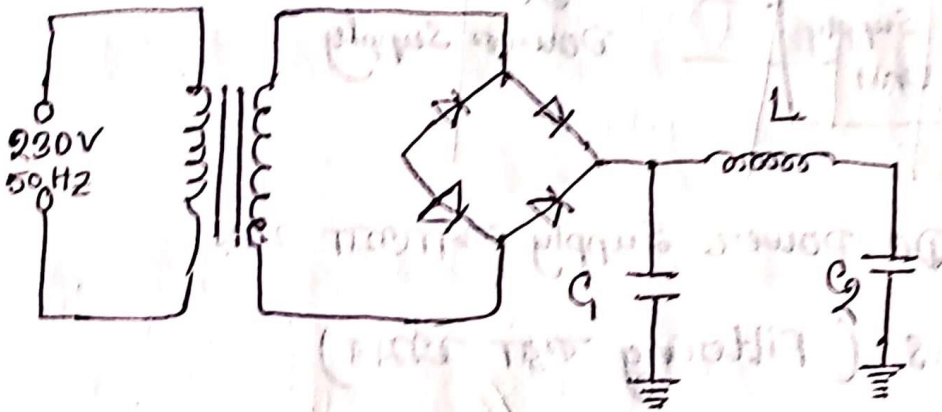


Fig:- Ordinary unregulated DC power supply circuit

⇒ The filter circuit removes the a.c component so that steady D.C voltage is obtained across the load.

Limitations:-

(1) If input (a.c) voltage increases by 5% then output d.c voltage also increases by 5%.

(2) Load current affects d.c output voltage.

(i) transformer windings (ii) rectifier (iii) filter circuit

causes voltage drop.

Voltage Regulation

The variation of output voltage the amount of load current drawn from the power supply is known as voltage Regulation.

$$\% \text{ voltage Regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$

V_{NL} = d.c. output voltage at no-load

V_{FL} = d.c. output voltage at Full load

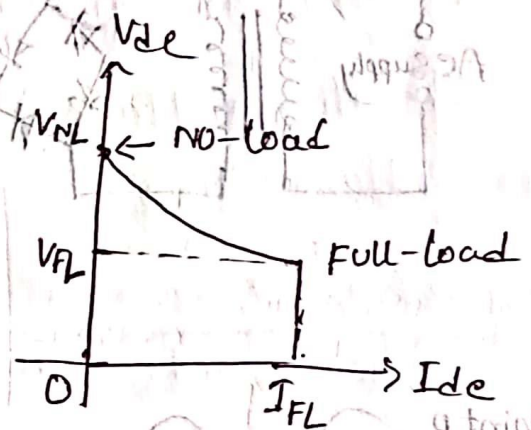
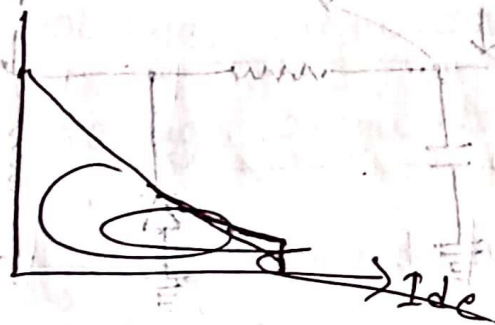


Figure:- voltage regulation curve

Minimum load Resistance:-

If a power-supply is required to deliver a full-load current I_{FL} at Full-load voltage V_{FL} , then




$$\text{Minimum load Resistance, } R_{L(\min)} = \frac{V_{FL}}{I_{FL}}$$

* If any attempt is made to decrease the value of R_L below this value, the stated d.c. output voltage

will not be available.

(math on this topic in -444 page) -446

Regulated Power Supply

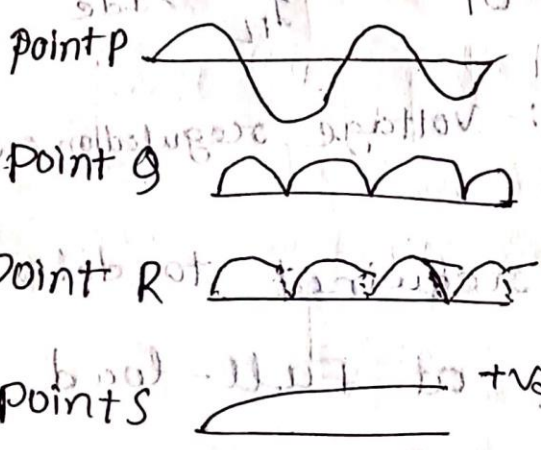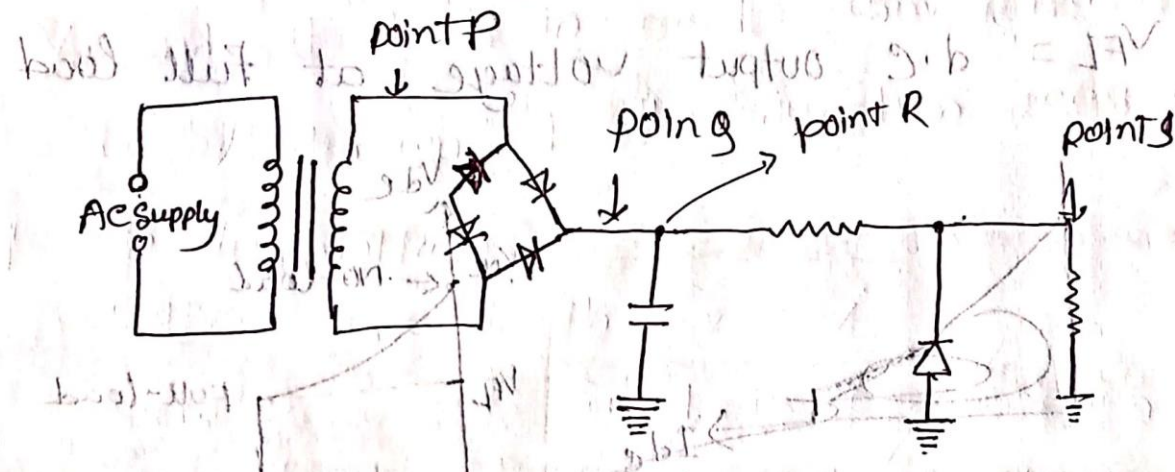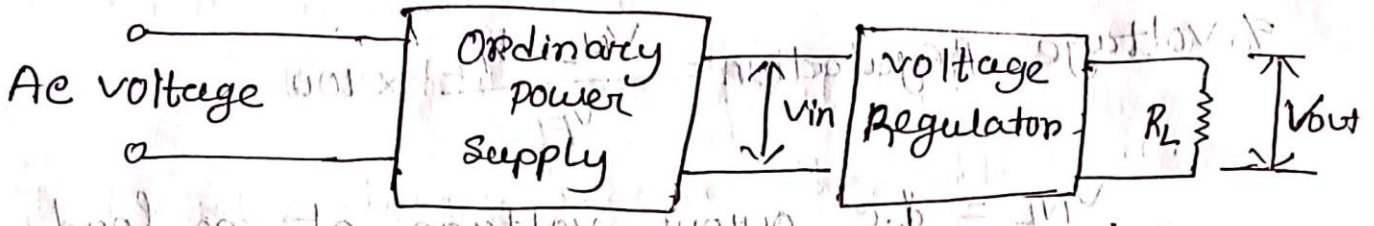

Bridge rectifier converts transformer secondary a.c voltage (point P) into pulsating voltage (point Q). Pulsating d.c voltage is applied to the capacitor filter, which reduces the pulsations in the rectifier d.c output voltage (point R). Then a Zener ^{voltage} regulator performs:

- (i) reduces the variations in the filtered output voltage.
- (ii) keeps output voltage (V_{out}) nearly constant whether

the load current changes or there is change in input & a.c voltage.



Types OF voltage Regulators

A device which maintains the output voltage of an ordinary power supply constant irrespective of load variations, or changes in input a.c voltage is known as voltage regulator.

There are two types of voltage regulators :-

(i) Series voltage regulator

(ii) Shunt voltage regulator

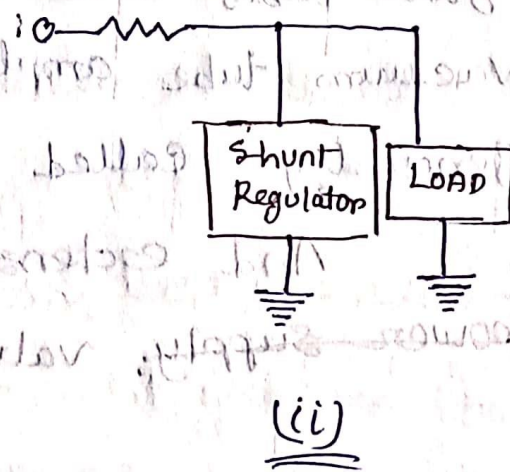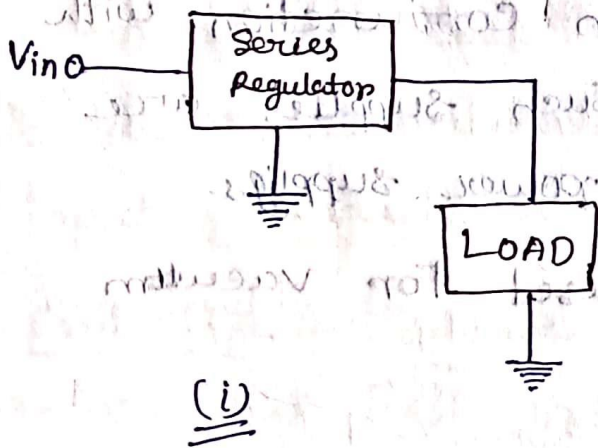

[1] For low voltages:-

D.C output voltages (upto 50V), either Zener diode alone or Zener in conjunction with transistor is used. Such supplies are called transistorised power supplies.

This can only give low stabilised voltages because the safe value 50 V. And if it is increased above this value the breakdown of the junction may occur!


[2] For High voltages:-

voltage greater than 50V

glow tubes are used in conjunction with vacuum tube amplifiers. Such supplies are generally called tube power supplies.

And extensively used for vacuum power supply valves.

17.5] Zener Diode Voltage Regulator

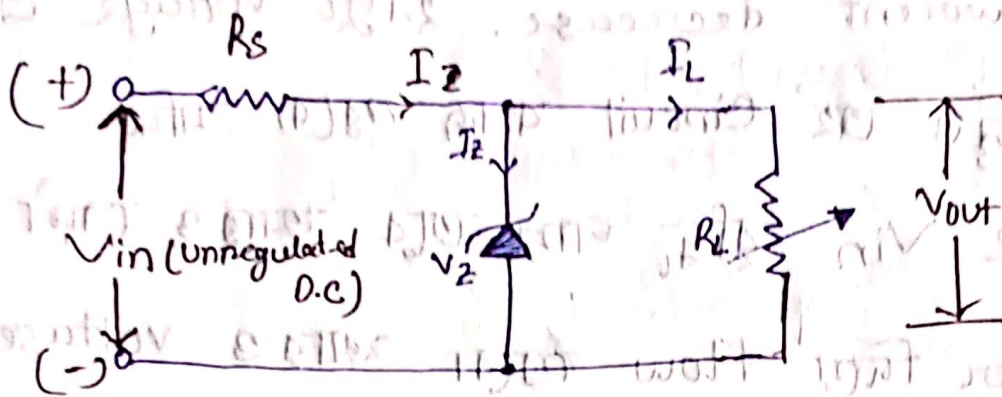

⇒ Breakdown or Zener Region - A Zener Diode operates in this region, the voltage across it is substantially constant for a large change of current through it. This is the characteristic of a voltage regulator.

V_{in} is greater than V_Z here. R_s with which is the series limiting resistance limits the input current.

Operations:- Zener maintains a constant voltage across the load in spite of changes in load current or input voltage. As load current increases, the Zener current decreases. So that, current through resistance R_s is constant.

As output voltage = $V_{in} - IR_s$, and I is constant.

Therefore, output voltage remains unchanged.

In reverse it would be true should the load current decrease. V_{in} I_L R_s V_L I_Z Z_Z V_Z V_{out}
দক্ষিণে V_{in} I_L R_s V_L I_Z Z_Z V_Z V_{out}
input voltage V_{in} I_L R_s V_L I_Z Z_Z V_Z V_{out}
current I_L R_s V_L I_Z Z_Z V_Z V_{out}
drop R_s V_L I_Z Z_Z V_Z V_{out}
শাঙ্ক। The reverse would be true should the
input voltage decrease.

Limitation:-

(i) It has low efficiency for heavy load currents.

It is because if the load current is large, there will be considerable power loss in the series limiting resistance.

(ii) The output voltage slightly changes due to Zener impedance as, $V_{out} = V_Z + I_Z Z_Z$,

changes in load current produce changes in Zener current. Consequently, the output voltage also changes. Therefore, the use of this circuit is limited to only such applications where

Variations in load current & input voltage are small.

17.6

Conditions for proper operation of Zener Regulator

(i) Zener must operate in the breakdown region:-

between $I_Z(\max)$ & $I_Z(\min) = 10\text{mA}$.

(ii) Zener has maximum dissipation break

जबि शकत। ता शल एरि destroy शक मावे।

$$P_Z(\max) = V_Z I_Z(\max)$$

$$I_Z(\max) = \frac{P_Z(\max)}{V_Z}$$

Math solve in (448) (449)

Transistor Series Voltage Regulator

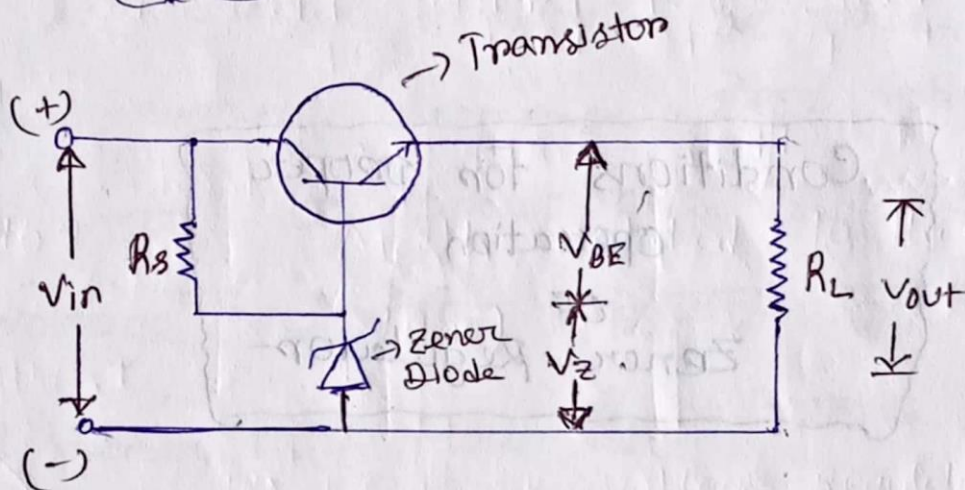


Figure:- Transistor series Voltage Regulator.

⇒ This circuit is called as series voltage regulator

because the load current passes through the series transistor Q_1 .

Here, Unregulated D.C power supply is fed to the input terminals & the regulated output is obtained across the load. The Zener diode provides the reference voltage.

Operation:-

The base voltage of transistor Q_1 is held to a relatively constant voltage across the Zener diode.

$$V_{out} = V_z - V_{BE}$$

① यदि output voltage कम, ~~है~~ the increased

base-emitter voltage causes transistor Q_1 to

Conduct more, thereby raising the output voltage.

As a result, the output voltage is maintained at a constant level.

② यदि output voltage बढ़े:-

base-emitter एर कम शान voltage transistor Q_1 एर उत्पादन कमाय, या output voltage को कमिटे हुन्छ।

Consequently, output voltage is maintained at a constant level.

③ The Advantage:-

~~This circuit~~ The changes in Zener current are reduced by a factor β . Therefore, the effect of Zener impedance is greatly reduced & much more stabilized output is obtained.

Limitation:

① Zener current एर परिचरन कमले ७, Output धुराकृति Constant शय ना। कारण, V_{BE} एर V_Z दुजम अन्तमात्रा वापार साथ साथ कम माय।

② Output voltage को जो मरके भाविकरण करवा
 मरके नम करवा न मरके कम किन्तु प्रदान करवा शक
 वा

(452 Math related to this
 topic)

E-201037
 SAKUR

Series Feedback voltage Regulator (454) Page

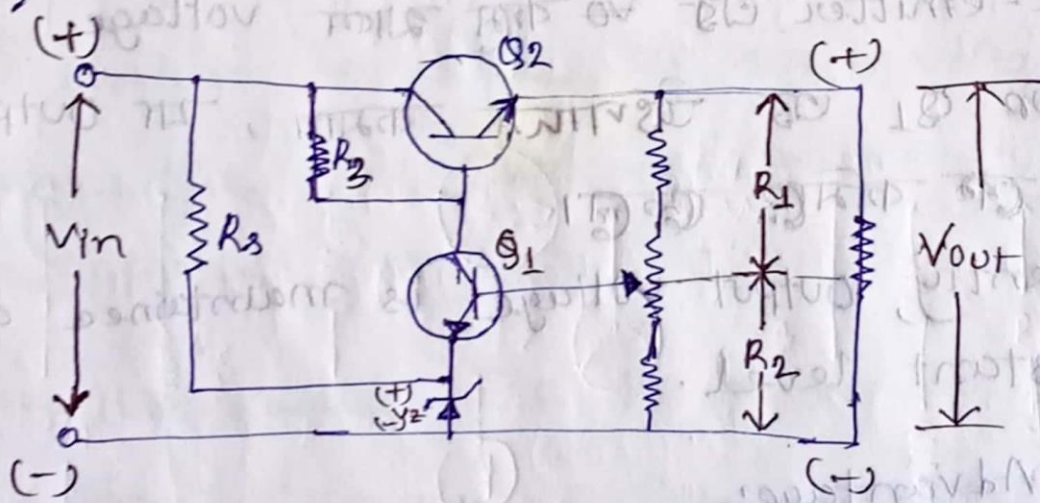


Figure:- Series Feedback voltage Regulator.

=> It employs principles of negative feedback to hold the output voltage almost constant despite changes in line voltage & load current.

Q2 is called pass transistor cause all load current passes through it.

There are the voltage divider that consists of R_1 & R_2 . The voltage divider samples the output voltage & delivers a negative feedback voltage to the base of Q_1 . The feedback voltage V_F controls the collector current of Q_1 .

Operations:

The unregulated D.C supply is fed to the voltage regulator. The circuit maintains constant output voltage irrespective of the variations in load or input voltage.

(i) Output voltage বেড়ে গেলে K_L region (R_2)

তে V_F voltage বেড়ে যায়। এর ফলে V_F Transistor (Q_1) এ feedback হয়। এবং সেখান

থেকে Q_1 এর collector current উৎপন্ন হয়।
কমিষ্টাকাল collector current R_2 এর মধ্য দিয়ে

মাড়ায়, Q_2 এর base voltage কমে যায়।
এর ফলে output voltage এর পরিমাণ

কমে যায় এবং অপ্রত্যাশিত voltage বাড়ে।
কিন্তু output voltage constant থাকে।

(ii) Output voltage যদি কমে যায়, feedback voltage V_F কমে যায়। এটি Q_1 এবং R_3 এর current কমিয়ে ফেলে। এর ফলে Q_2 এর Base voltage এবং Output voltage ও বাড়ে।
 -এভাবেই output voltage original level এ থাকে।

17.9 Short-Circuit Protection:-

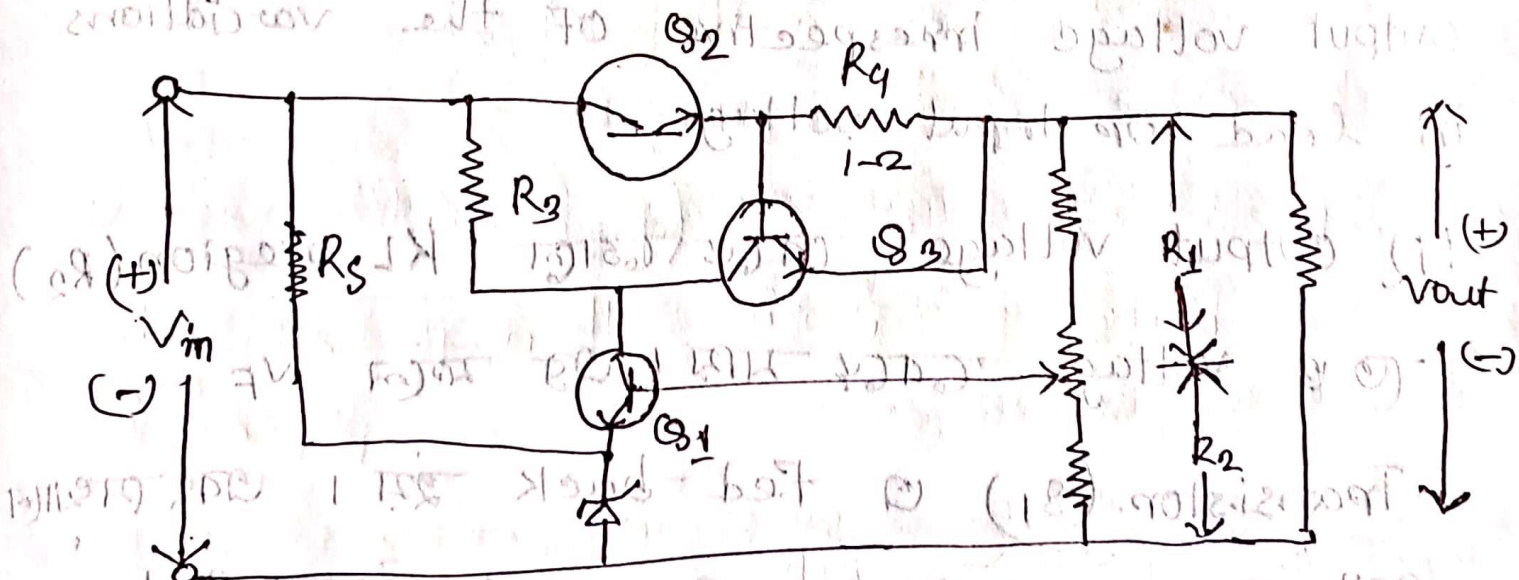


Fig: Short circuit protection

⇒ The pass transistor can be destroyed by excessive load current if the load is accidentally shorted, in any series circuit.

So, a current limiting circuit is added to a series regulator.


And it is consisted with a transistor (Q_3) & a series resistor (R_4) in between base & emitter terminals.

Operation:-

(i) Load current কম থাকলে, voltage R_4 ছোট হবে এবং Q_3 বন্ধ থাকবে।
এই condition এ circuit সার্ভিস হয়ে কাজ করবে।

(ii) যদি load current অতিরিক্ত বেড়ে যায়, R_4 এর voltage বেড়ে যায় যা Q_3 কে চালু করে ফেলে। Q_3 এর collector current R_3 এর দিকে যেতে থাকে। যা Q_2 এর base voltage কমিয়ে ফেলে। Base voltage এর কম মাওয়া pass transistor এর উৎপাদন কমিয়ে ফেলে, load current এর বৃদ্ধি বা হ্রাস।
যাতে load current সার্ভিসে $700mA$ এর মতো হয়।

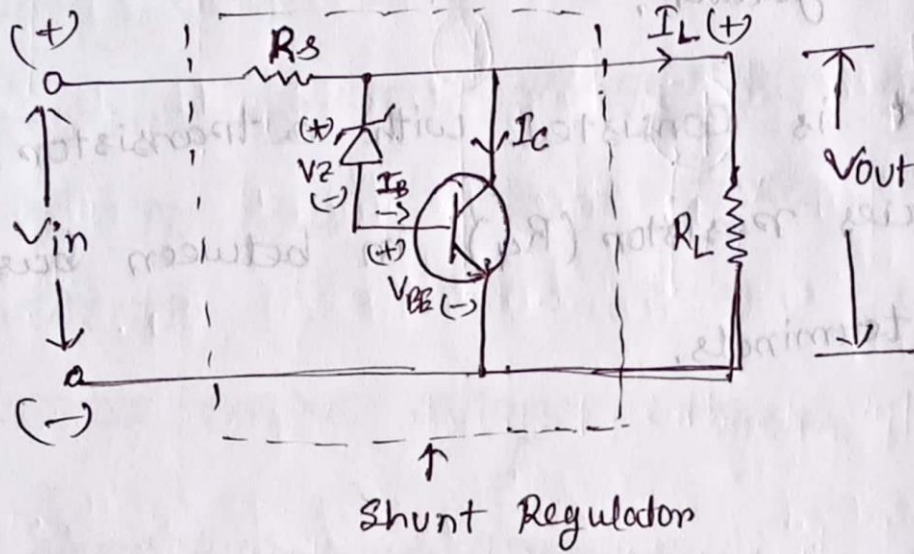17.10 Transistor Shunt Voltage Regulator:-



Output voltage, $V_{out} = V_Z + V_{BE}$

\swarrow Zener voltage \searrow Transistor Base-emitter

\Rightarrow The voltage drop across series resistance depends upon the current supplied to the load R_L .

- যদি load Resistance কম, transistor এর base এর current ও কম মাস। যার ফলে খুব কম পরিমাণ current shunt করা হয়।

- মধ্য আর মধ্য, Load current বেশি হয়, তখন regulated voltage load এর দিকে maintain করা হয়। বিপরীত হলে load resistance বেড়ে যায়।

(i) A large portion of the total current through R_s flows through transistor rather than to the load.

(ii) There is considerable power loss in R_s .

(iii) There are problems of overvoltage protection in this circuit.

एक श्रृंखला, श्रृंखला वोल्टेज रेगुलेटर 250 series voltage regulator @ prefer

वोल्टेज रेगुलेटर

17.11

Shunt Feedback Voltage Regulator

Page:-457

P.T.O

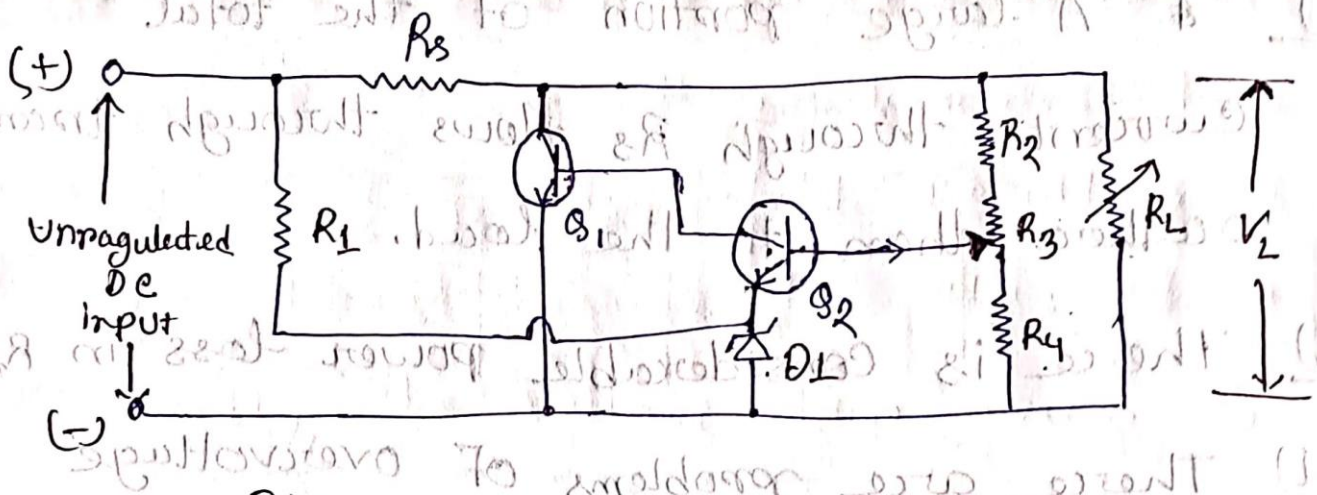


Figure:- Shunt Feedback Voltage Regulator.

⇒ This circuit is an improved form of the simple series voltage regulator.

(Sample circuit is a simple voltage divider

circuit $(R_2 - R_3 - R_4)$). In a shunt feedback voltage regulator, the output from the sample &

reference circuits are applied (It is made

up of Zener D_1 & R_1 & derives the reference voltage from the unregulated D.C input voltage)

are applied to the error detector/amplifier

Q_2 . The output from Q_2 controls the conduction

current through the shunt transistor Q_1 to

maintain the constant load voltage V_L .

17.12 Glow Tube Voltage Regulator (Zener circuit)

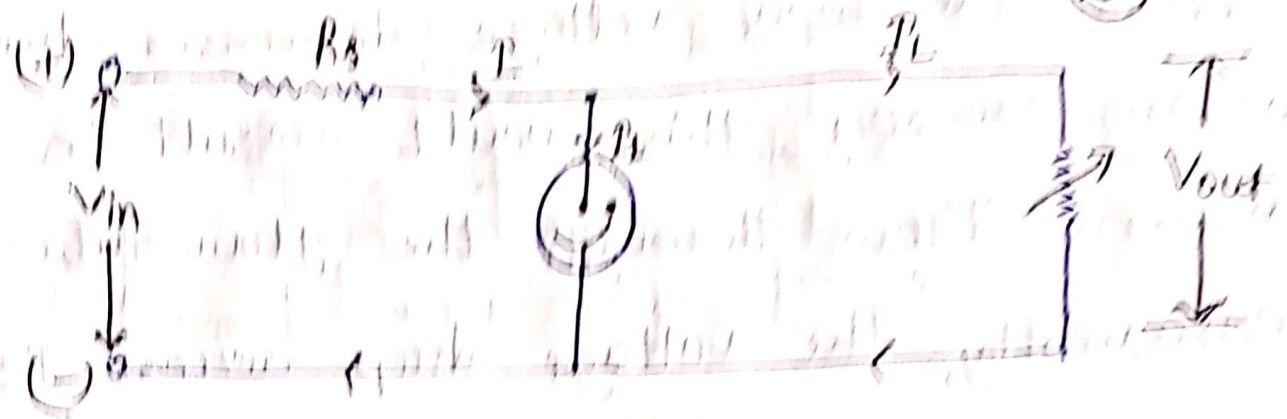


Figure: Glow Tube Voltage Regulator.

⇒ This will maintain constant voltage across the load in spite of changes in load current or input voltage. Now, should the load decrease, the output voltage would tend to increase.

The glow tube will draw more current without any increase in the output voltage. The drop in load current is offset by the increase in tube current, and the current through R_s remains constant. As output voltage $= V_{in} - I R_s$, therefore, output voltage remains unchanged.

Similarly, the circuit will maintain constant

output voltage, if the input voltage changes. Suppose, the input voltage decreases due to any reason, this would result in less current flow through the glow tube. Consequently, the voltage drop across R_s decreases, resulting in constant voltage across the load.

17.13

Series Triode Voltage Regulator

Page
- 459

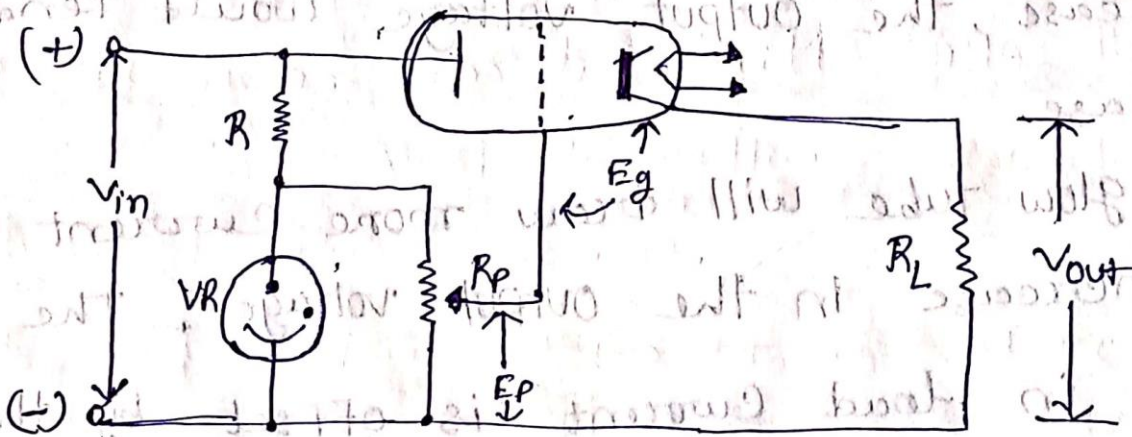


Figure: Series Triode Voltage Regulator.


It is similar to series transistor regulator except that here triode & glow tube are used instead of transistor & Zener diode.

The resistance R & glow tube (V.R.) help to maintain constant potential across the load. A potentiometer R_p is connected across the glow tube & its variable point is connected to the grid of the circle.

17.14


Series Double Triode voltage Regulators

Page 2-459

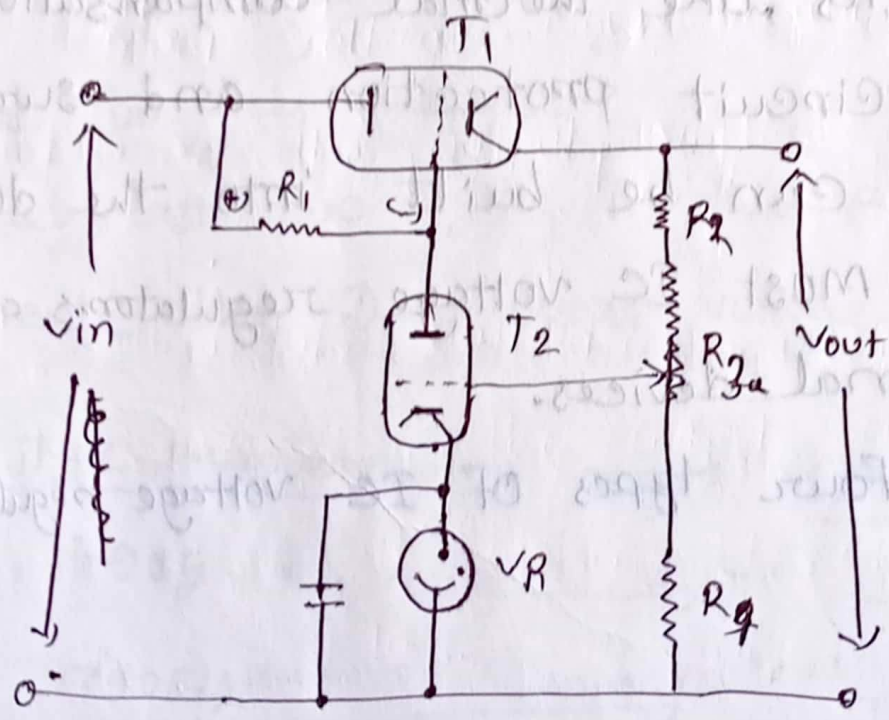

[17.15]

[IC Voltage Regulators]

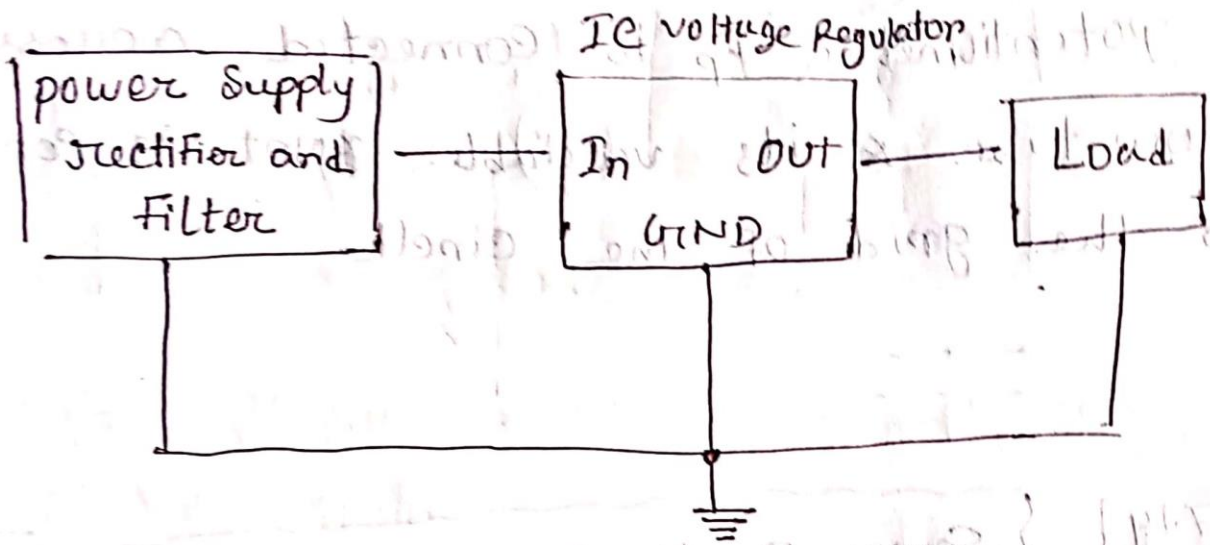

⇒ One advantage of IC voltage regulators is that properties like thermal compensation, short ~~case~~ circuit protection and surge protection can be built into the device.

Most IC voltage regulators are three-terminal devices.

There are four types of IC voltage regulators:


[P.T.O]



1) Fixed positive voltage regulators

7800 series of IC regulators is the most popular. The last two digits in the part number indicate the D.C. output voltage.

Type number	→	Output voltage
→ 7812	→	+12.0 V
→ 7824	→	+24.0 V

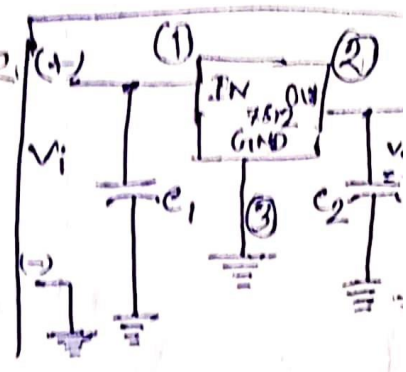


2) Fixed Negative voltage Regulators


The 7900-series of IC regulators is commonly used for this purpose.

Here last two digits in the part number indicate the D.C. output voltage.

Type Number	→	Output Voltage
7905	→	-5.0 V
7905.2	→	-5.2 V

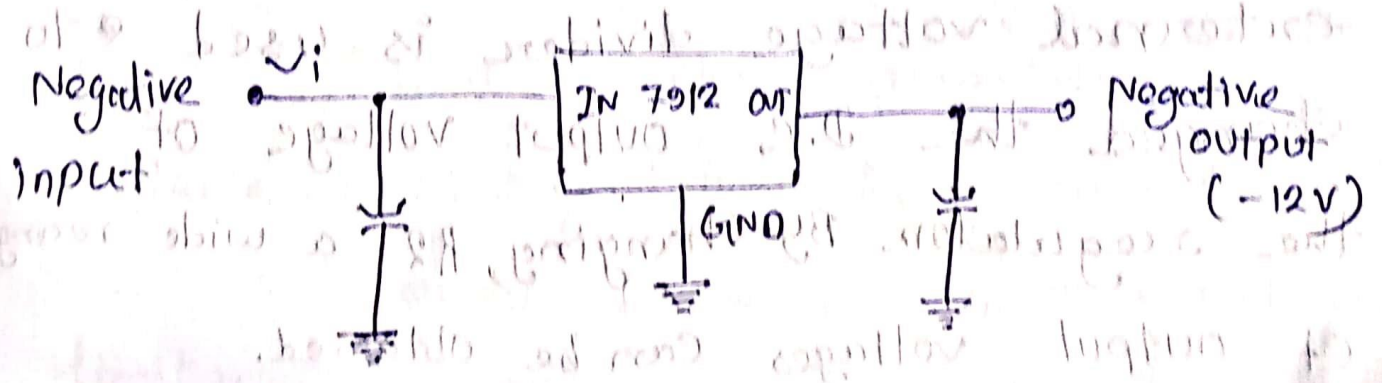

③ Adjustable Voltage Regulator

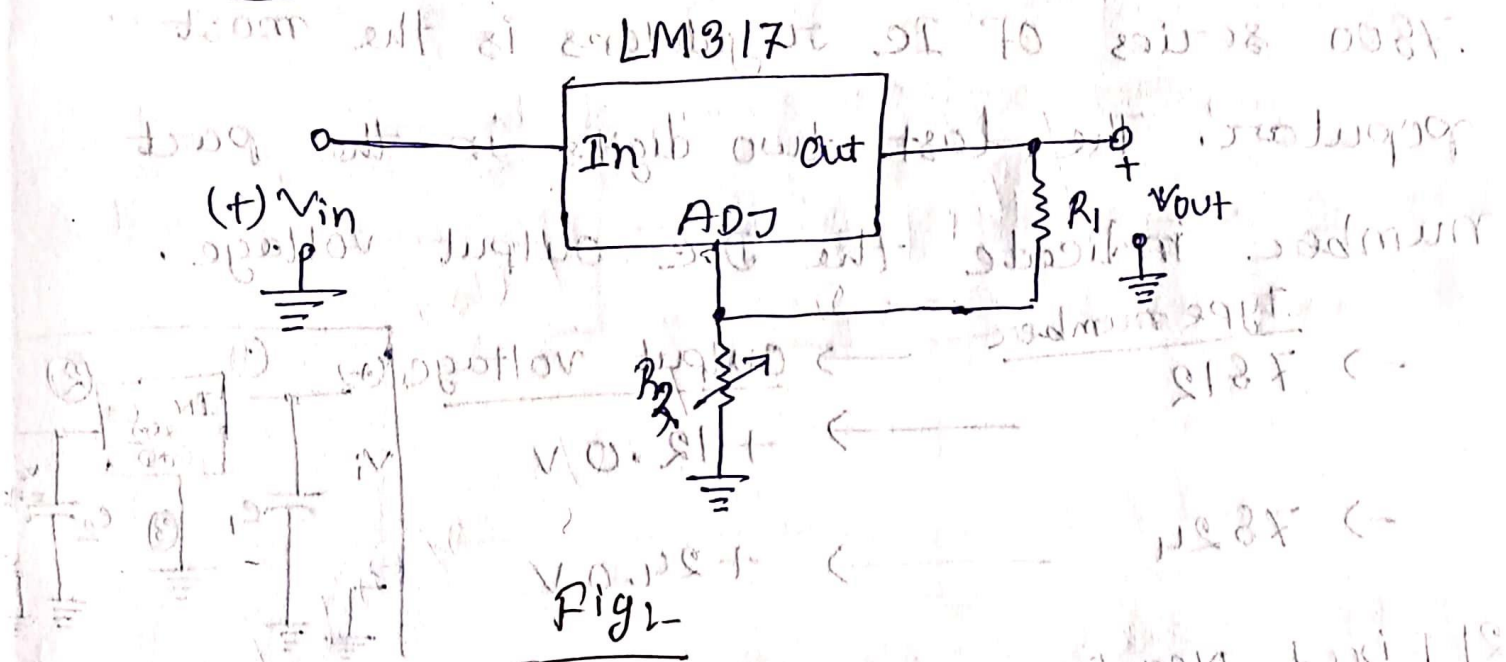

⇒ The adjustable voltage regulator can be adjusted to provide any D.C. output voltage that is within its two specified limits.

• The most popular three terminal IC

adjustable voltage regulator is the LM317.

It has an input terminal, output terminal

and an adjustment terminal. An


external voltage divider is used to

change the D.C. output voltage of

the regulator. By changing, R_2 a wide range of output voltages can be obtained.

4] Dual-Tracking Voltage Regulator:-

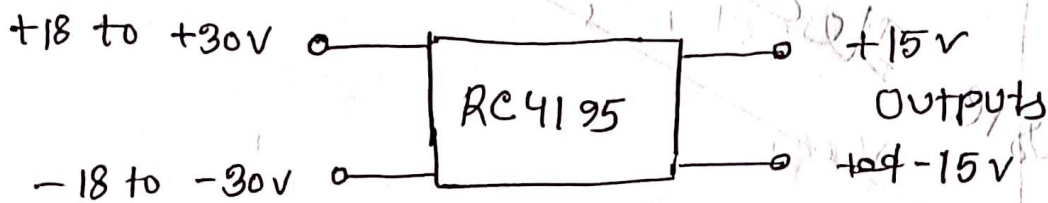This provides equal positive & negative output voltages. This is used when split-supplied voltages are needed.



→ Circuit: RC4195 IC

⇒ Input:- Pos:- +18V to +30V

Neg:- -18V to -30V

⇒ Output:- +15V or,
-15V

⇒ Output Current: 150 mA for each

supply & a load regulation of 3mV.

Adjustable dual tracking regulators are also available. These regulators have outputs that can be varied between their two rated limits.